

HIGH-PERFORMANCE
SIGNAL & POWER INTEGRITY

HIGH-PERFORMANCE
IC DESIGN & VERIFICATION

FIRST-PASS
SYSTEM
SUCCESS

APPLICATION WORKSHOPS FOR
HIGH-PERFORMANCE ELECTRONIC DESIGN

*System Optimization of
Motor Resolver
including Drive Circuitry
and Cable Parasitics*

Ansoft Corporation

HIGH-PERFORMANCE
RF & MICROWAVE

HIGH-PERFORMANCE
ELECTROMECHANICAL SYSTEMS



Abstract

- Resolver as an angular position sensor is widely used
- Resolver system is complicated, equation based method is insufficient
- Resolver normally operates in the environment that has EMI/EMC issue
- Fast response and accurate position feedback is critical in the electrification of automotives and aircrafts
- A system level circuit simulator is needed to accurately account for all the above-mentioned factors



Outline


- Variable Reluctance Resolver FEA Model
- Resolver Excitation Signal Generator
- Resolver-to-Digital Converter
- Ideal Resolver System Behavioral Model
- Resolver Cable Parasitics
- Resolver System Integration
- Conclusions



Resolver System Simulation

Simplorer, Q3D, Maxwell, DSO, Optimetrics

Simplorer as System Simulator




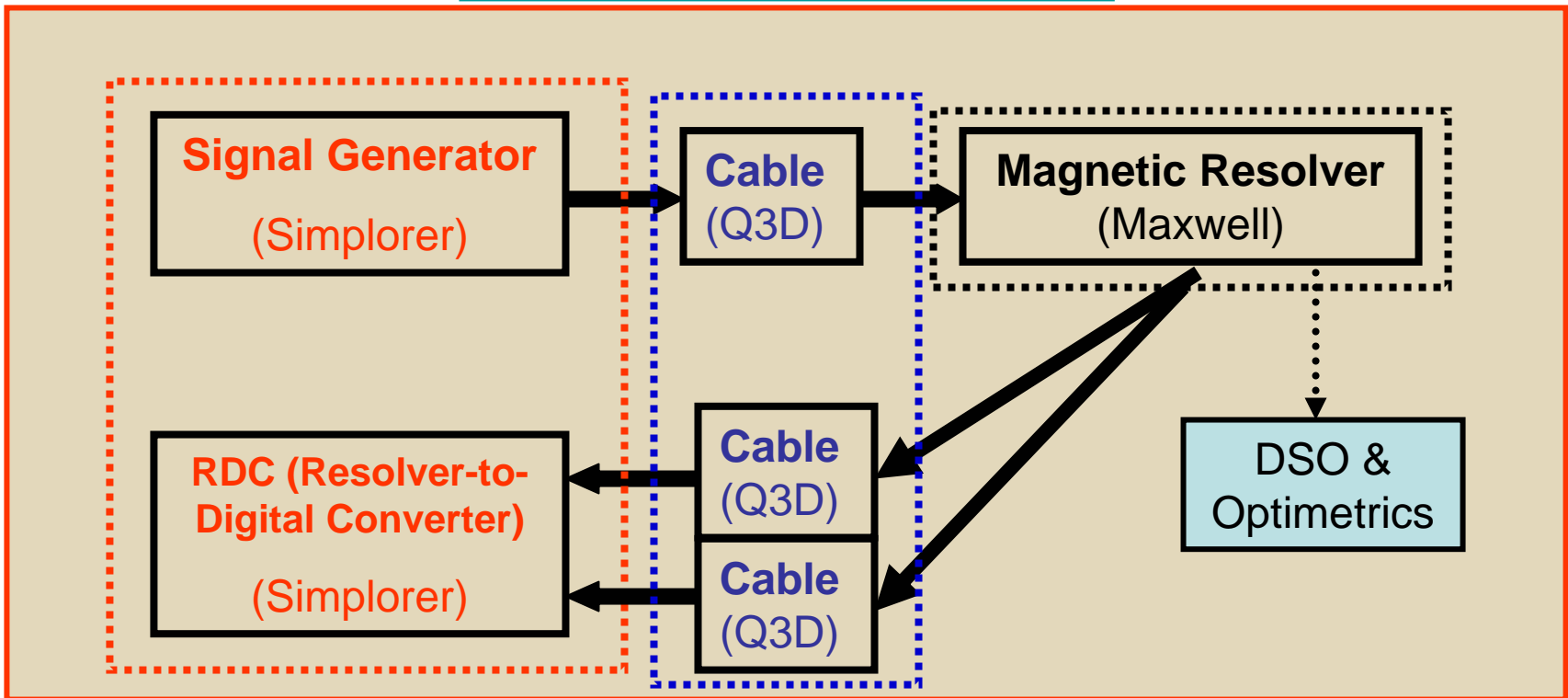


Advantages of Resolver over Optical Encoder




- Higher Resolution (up to 16-bit)
- Wider Environment Temperature (-55~+220°C max)
- Higher Tolerance to Vibration (20~40g's)
- Higher Tolerance to Dust
- Robust EMC/EMI Performance(no electronics on board, cab be shielded)
- More Sizes Available



Resolver FEA Model

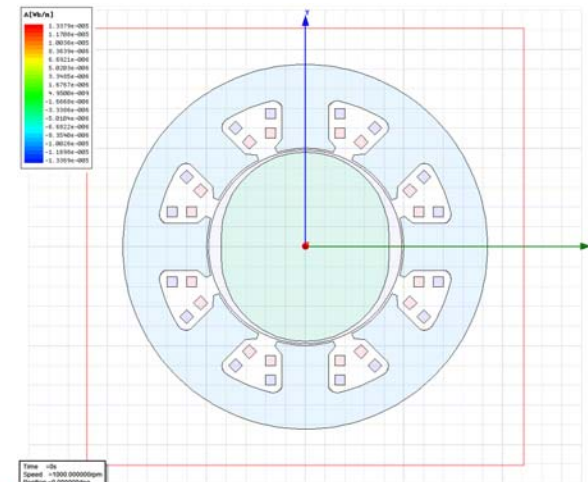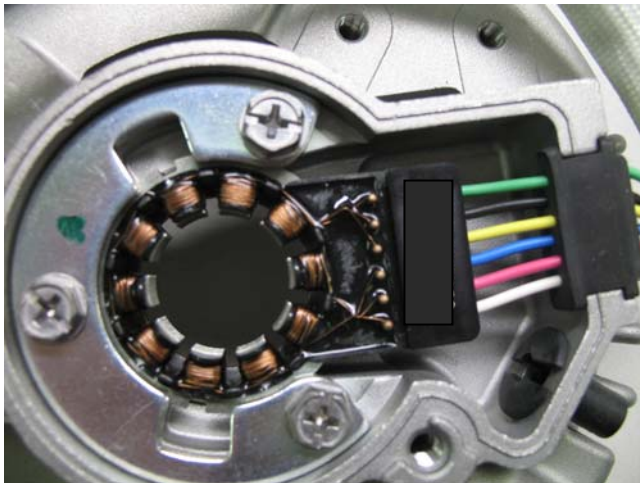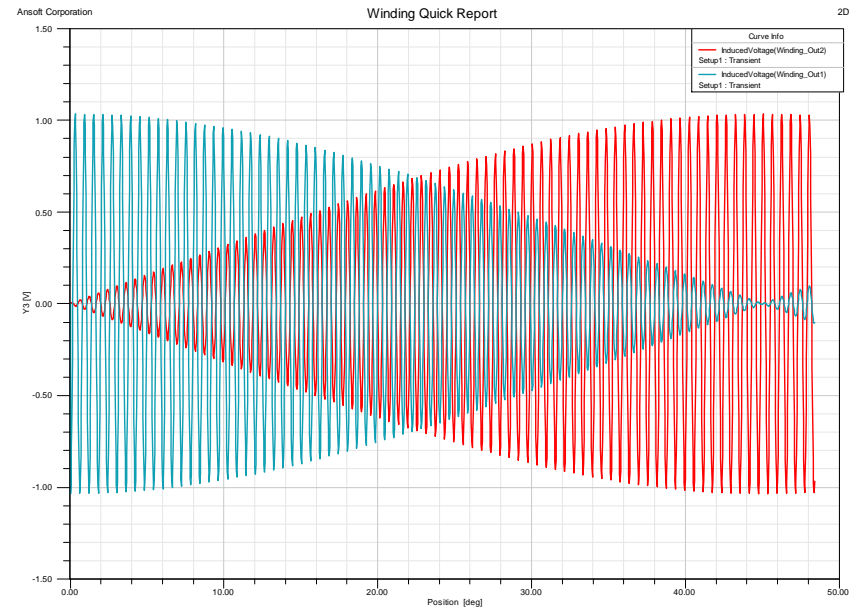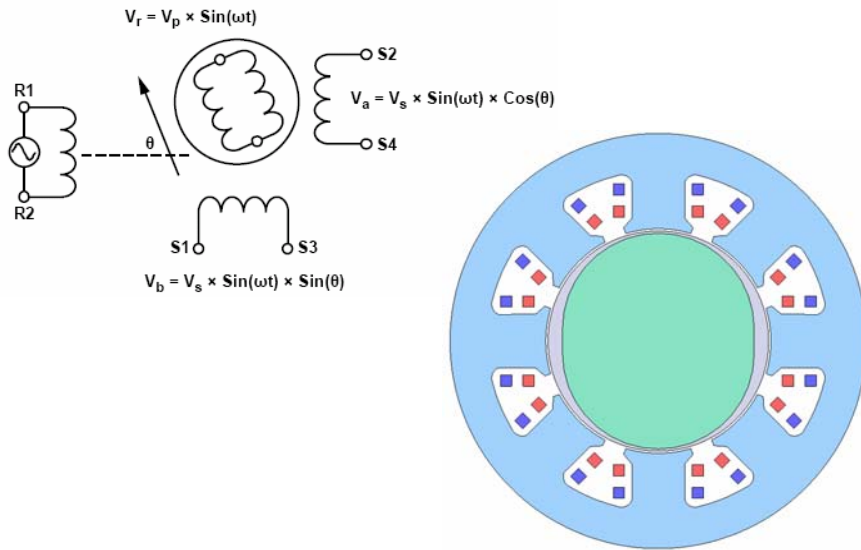


Resolver Design Optimization

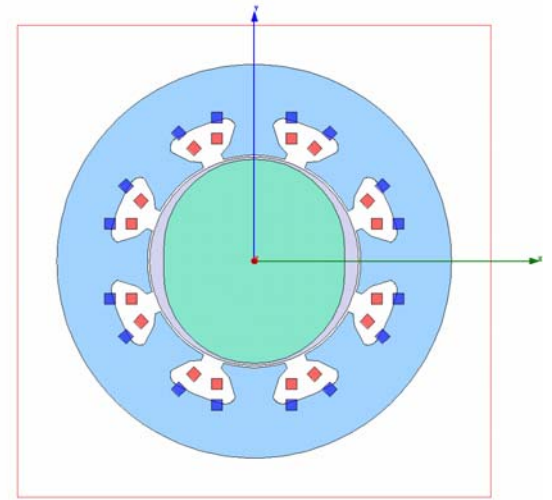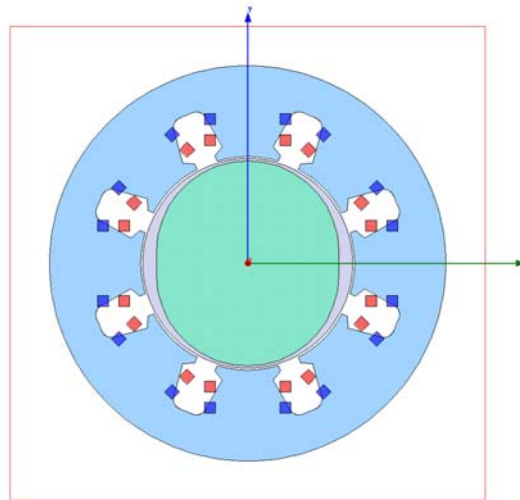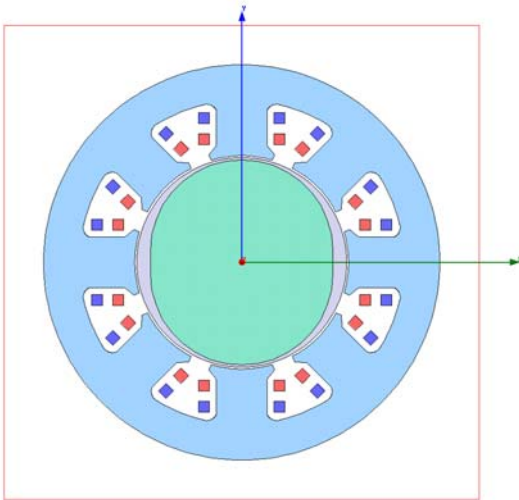


- Parametric Sweep Geometry
- Sweep Number of Turns in the Slots
- Check Different Winding Arrangements
- Try Different Materials
- Innovate New Designs
- Etc.

Goal:

- * Optimize Outputs
- * Reduce Cost

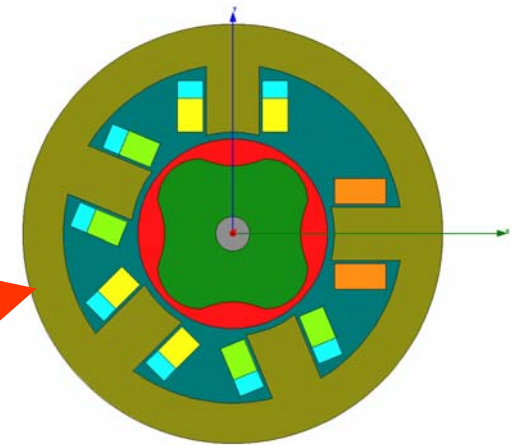


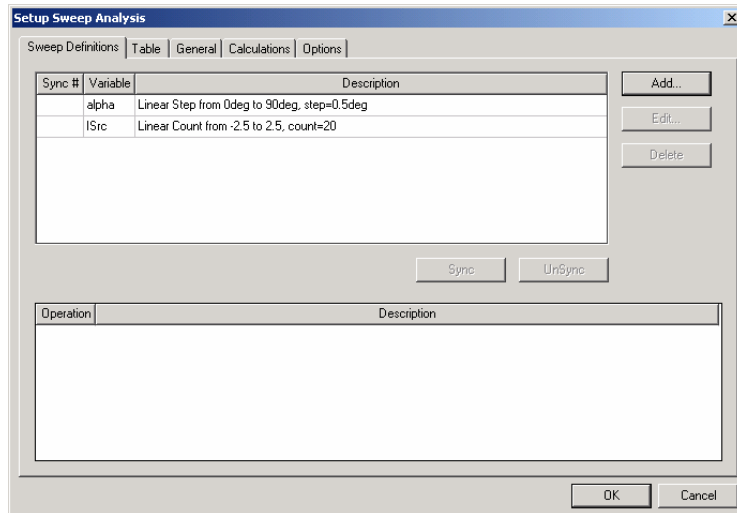Creating an Equivalent Circuit Model for the Resolver



Sweep Angle (0~90 deg, in steps of 0.5 deg)
Sweep Source Magnitude (-2.5~2.5 Amp Turns, 20 counts)
Total: $181 * 20 = 3,620$ rows
Each row takes 50 seconds to simulate
Total simulation time on one machine = 181,000 seconds

50.28 Hours!

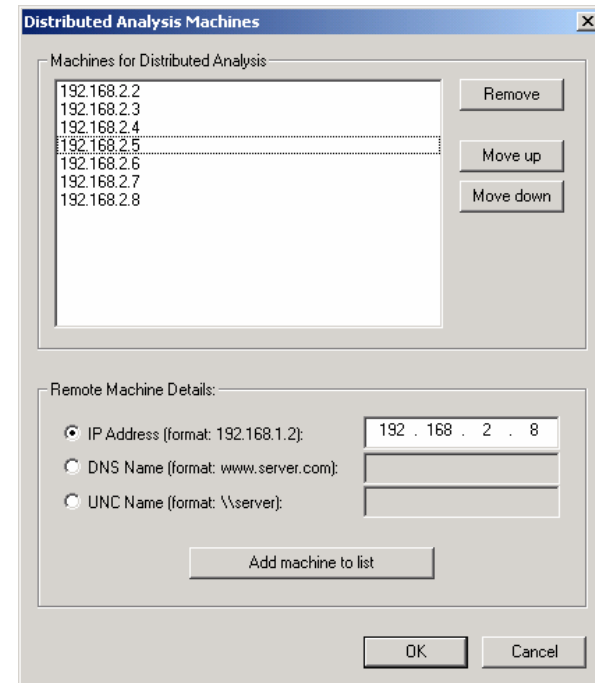

Use DSO (Distributed Analysis)
8 Machines were used
Simulation Time = 9 Hours 10 Minutes

Almost 6 Times!



Create an Equivalent Circuit Model for the Resolver

Post Analysis Display

ParametricSetup1




Result | Profile

View: Table Show complete output name

Plot

Variation	ISrc	alpha	Matrix1.MagFlux(Out1)...	Matrix1.MagFlux(Out2)...	Matrix1.MagFlux(Sourc...	Torq
19	2.23684210526316	0deg	-0.0030111001448073...	4.91388773970795e-0...	0.0164237739003006...	-2.204
20	2.5	0deg	-0.0033653472482377...	5.49199221353579e-0...	0.0183559826429141...	-2.753
21	-2.5	0.5deg	0.00335715350787347...	-6.10334820072163e-0...	-0.0183226757406397...	4.117
22	-2.23684210526316	0.5deg	0.0030037689036335...	-5.46089044455704e-0...	-0.0163939729881088...	3.296
23	-1.97368421052632	0.5deg	0.00265038430754638...	-4.81843270501859e-0...	-0.0144652702499072...	2.566
24	-1.71052631578947	0.5deg	0.00230073160065879...	-4.2932668249699e-00...	-0.0125549367115618...	1.492
25	-1.44736842105263	0.5deg	0.00194672288224681...	-3.63276421368784e-0...	-0.010623407968034wb	1.068
26	-1.18421052631579	0.5deg	0.00159281416914345...	-2.9722616137928e-00...	-0.0086918792338420...	7.152
27	-0.921052631578947	0.5deg	0.00123888546038464...	-2.31175902322843e-0...	-0.0067603505072893...	4.326
28	-0.657894736842105	0.5deg	0.00088489675500457...	-1.65125643996121e-0...	-0.0048288217866774...	2.207
29	-0.394736842105263	0.5deg	0.00053093805203732...	-9.90753861895159e-0...	-0.0028972930703087...	7.947
30	-0.131578947368421	0.5deg	0.00017697935051812...	-3.3025128695439e-0...	-0.0009657643564866...	8.830
31	0.131578947368421	0.5deg	-0.0001769793505182...	3.30251286957799e-0...	0.00096576435648676...	8.830
32	0.394736842105263	0.5deg	-0.0005309380520372...	9.90753861892694e-0...	0.00289729307030875...	7.947

Export... Apply Revert Close

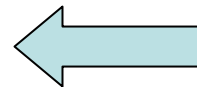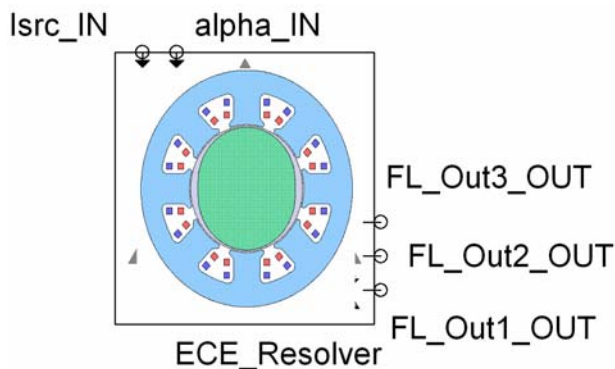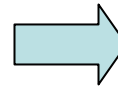

```

Resolver_ECE.sml
// BEGIN ANSOFT HEADER
// node N_1 FL_Out1_OUT
// node N_2 FL_Out2_OUT
// node N_3 FL_Out3_OUT
// node N_4 ISrc_IN
// node N_5 alpha_IN
// Format: SML
// Pin Layouts:
// Left:
// Right: FL_Out1_OUT FL_Out2_OUT FL_Out3_OUT
// Model: Lookup Table
// END ANSOFT HEADER
//
MODELDEF Resolver_ECE
(
// Interface Nodes
PORT real in: ISrc_IN;
PORT real in: alpha_IN;
PORT real out: FL_Out1_OUT = nOUT1.V;
PORT real out: FL_Out2_OUT = nOUT2.V;
PORT real out: FL_Out3_OUT = nOUT3.V;

// Extra Input Calculations
INTERM E Ein1 N1:=GND, N2:=nIN1 \
{EMF:=ISrc_IN, AC_MAG:=0, PARTDERIV:=1};
INTERM VM Vin1 N1:=nIN1, N2:=GND;
INTERM E Ein2 N1:=GND, N2:=nIN2 \
{EMF:=alpha_IN, AC_MAG:=0, PARTDERIV:=1};
INTERM VM Vin2 N1:=nIN2, N2:=GND;

// Extra Output Calculations
INTERM VM Vout1 N1:=nOUT1, N2:=GND;
INTERM VM Vout2 N1:=nOUT2, N2:=GND;
INTERM VM Vout3 N1:=nOUT3, N2:=GND;

// Piecewise-Linear Lookup Table
INTERM NDSRC Ptable NO:=nOUT1, N1:=GND, N2:=nOUT2, N3:=GND, \
N4:=nOUT3, N5:=GND \
{QUANT:={nIN1.V, nIN2.V}, \
SRC:={VSRC, VSRC, VSRC}, \
TableData:=".MODEL test pwl TABLE={ \
20, -2.5, -2.23684, -1.97368, -1.71053, -1.44737, \
-1.18421, -0.921053, -0.657895, -0.394737, -0.131579, 0.131579, \
0.394737, 0.657895, 0.921053, 1.18421, 1.44737, 1.71053, \
1.97368, 2.23684, 2.5, 0, 181, 0, \
0.5, 1, 1.5, 2, 2.5, 3, \
3.5, 4, 4.5, 5, 5.5, 6, \
6.5, 7, 7.5, 8, 8.5, 9, \
9.5, 10, 10.5, 11, 11.5, 12, \
12.5, 13, 13.5, 14, 14.5, 15, \
15.5, 16, 16.5, 17, 17.5, 18, \
18.5, 19, 19.5, 20, 20.5, 21, \
21.5, 22, 22.5, 23, 23.5, 24, \
24.5, 25, 25.5, 26, 26.5, 27, \
27.5, 28, 28.5, 29, 29.5, 30, \


```







Resolver System Simulation

Simplorer, Q3D, Maxwell, DSO, Optimetrics

Simplorer as System Simulator

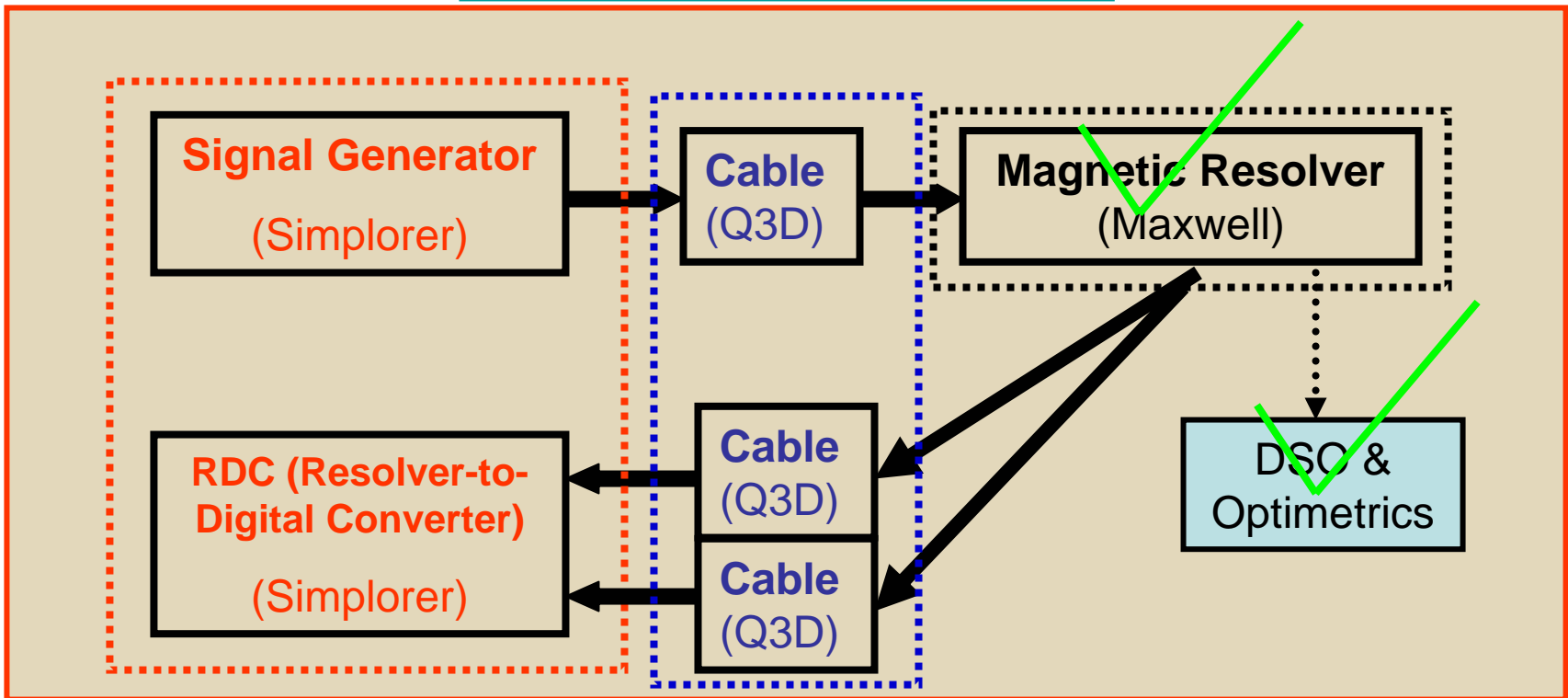

Resolver Excitation Signal Generator

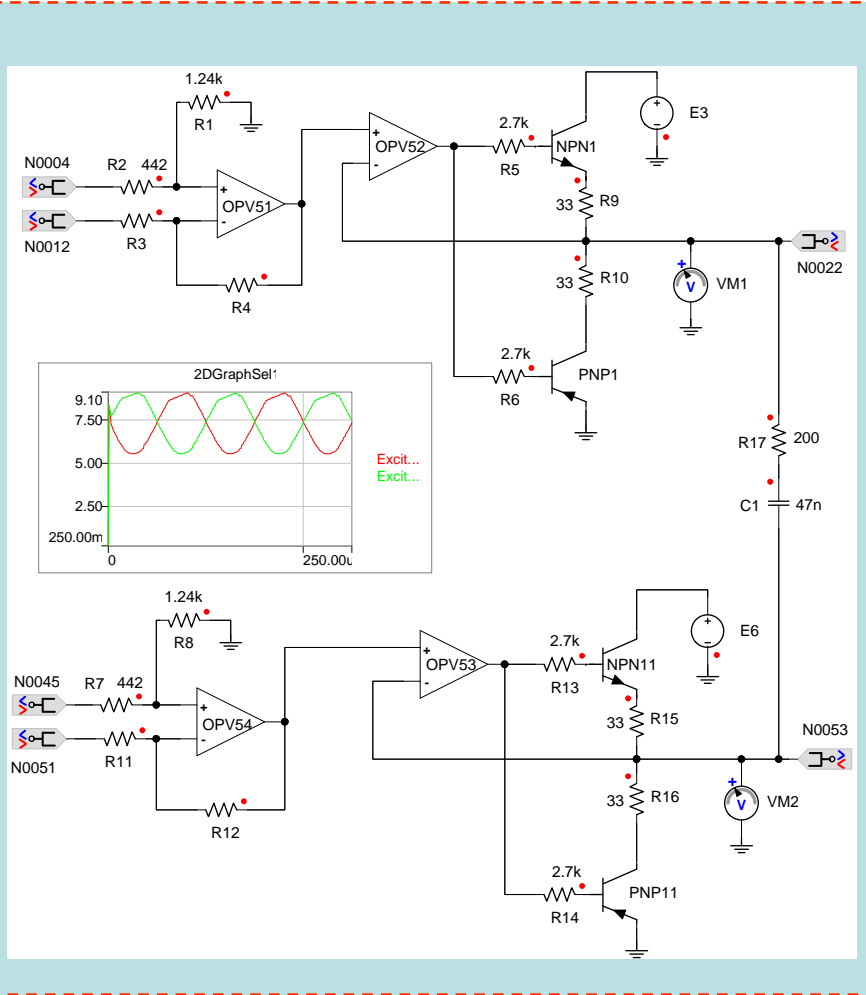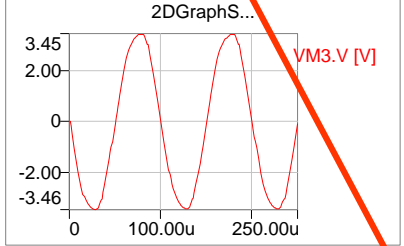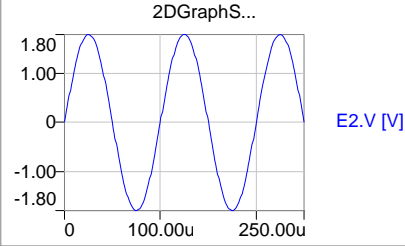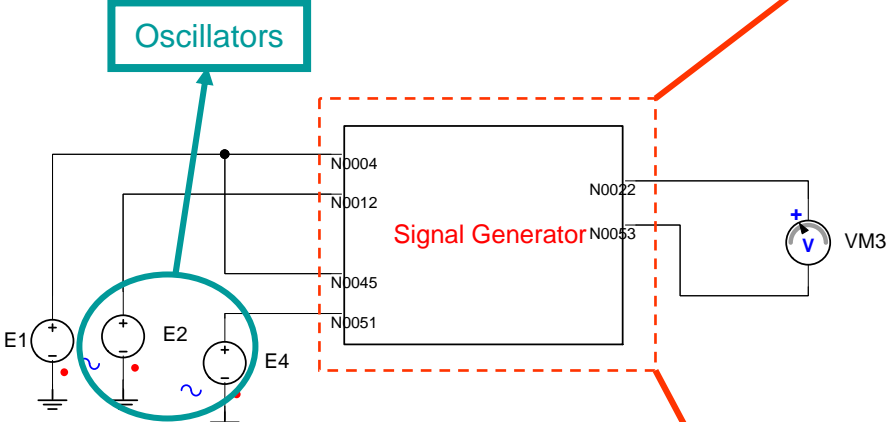


Signal Generator Sub-circuit



Resolver System Simulation

Simplorer, Q3D, Maxwell, DSO, Optimetrics

Simplorer as System Simulator

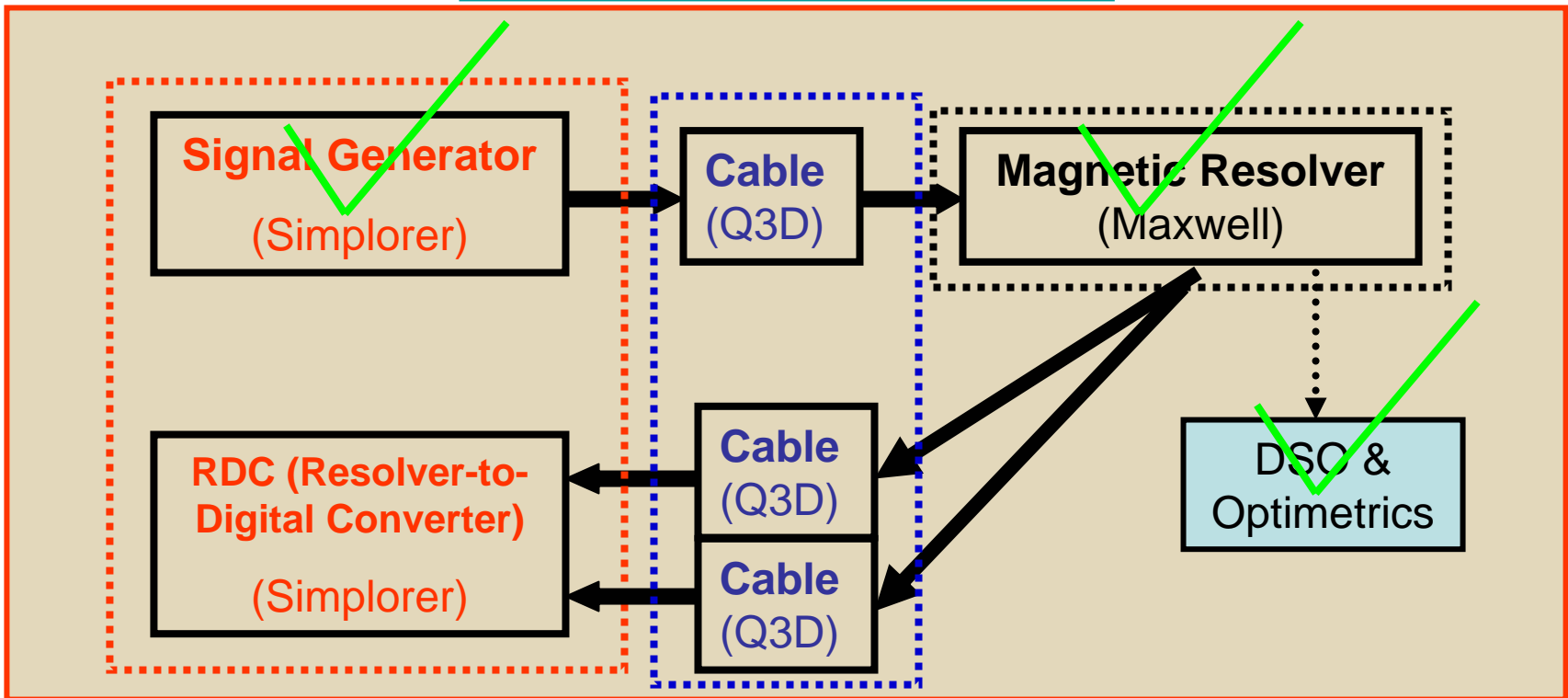

Resolver-to-Digital Converter

Classical RDC Algorithm

Resolver:

$$V_{excitation} = U1 * \sin(2 * \pi * Freq * t)$$

$$V_{Out_Sin} = U2 * \sin(2 * \pi * Freq * t) * \sin(\text{Thita})$$

$$V_{Out_Cos} = U2 * \sin(2 * \pi * Freq * t) * \cos(\text{Thita})$$

RDC:

90 Degree Phase shift:

$$V_{Out_Sin_1} = U2 * \sin(2 * \pi * Freq * t + 90 \text{deg}) * \sin(\text{Thita})$$

$$= U2 * \cos(2 * \pi * Freq * t) * \sin(\text{Thita})$$

Summation:

$$V_{sc} = V_{Out_Sin_1} + V_{Out_Cos}$$

$$= U2 * \sin(2 * \pi * Freq * t + \text{Thita})$$



Magnitude Match:

$$V_{sc_1} = U1 * \sin(2 * \pi * Freq * t + \text{Thita})$$

Comparison:

$$V_{excitation} = U1 * \sin(2 * \pi * Freq * t)$$
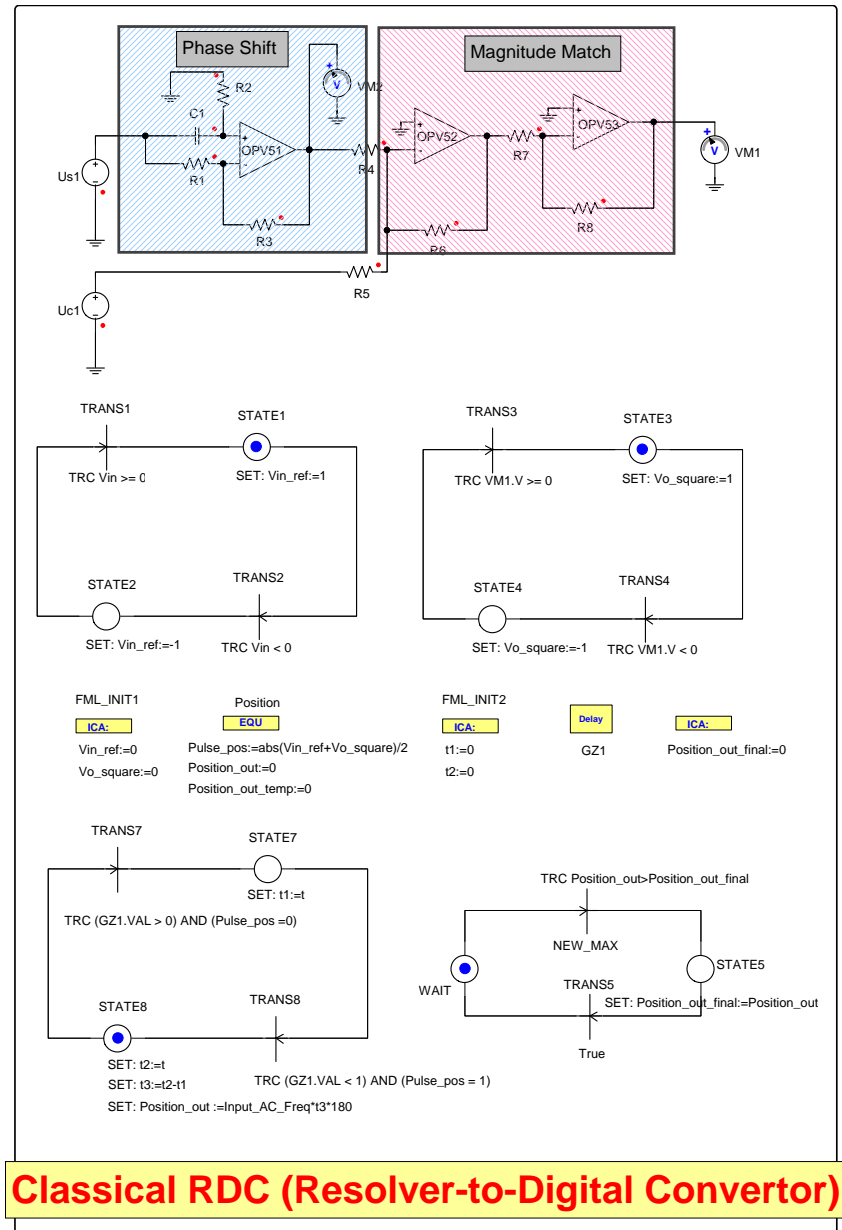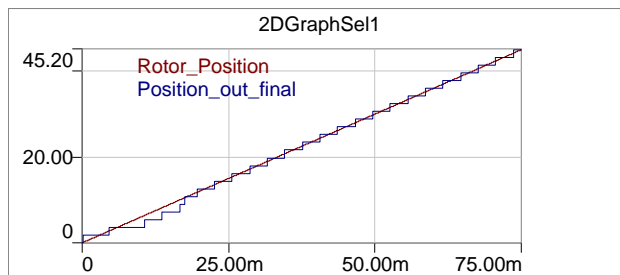
$$V_{sc_1} = U1 * \sin(2 * \pi * Freq * t + \text{Thita})$$




Classical RDC (Resolver-to-Digital Converter)





Resolver-to-Digital Converter (continued)

FUNCTIONAL BLOCK DIAGRAM

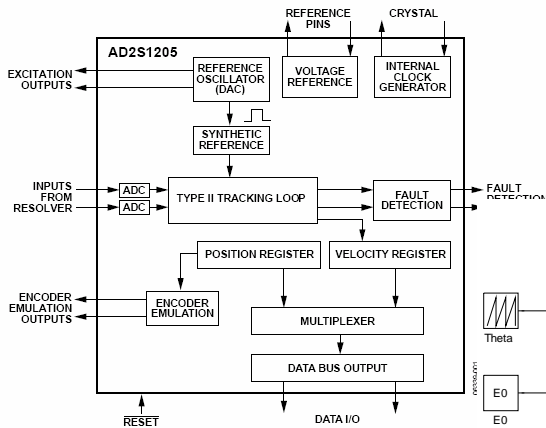

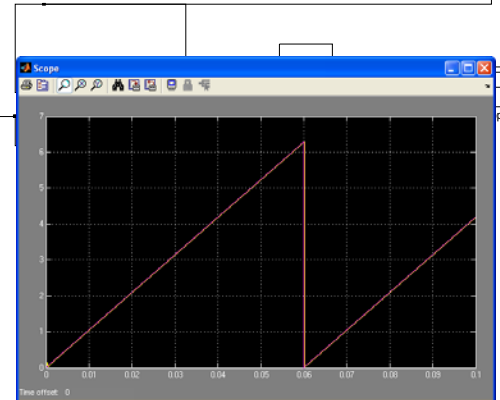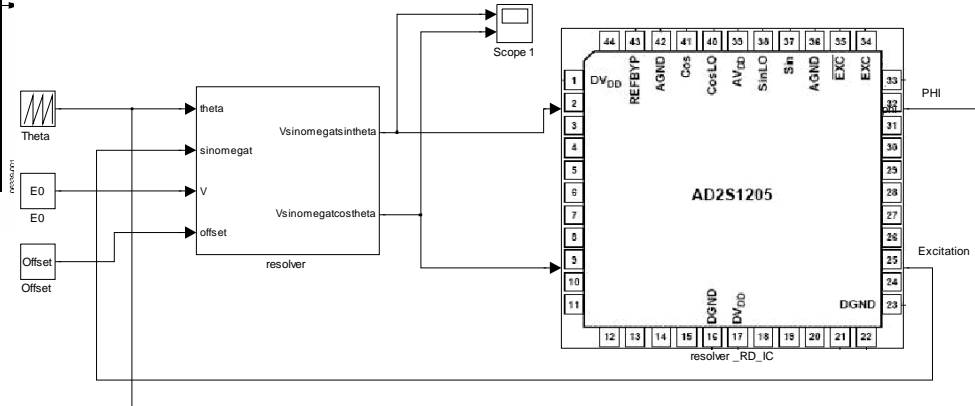(Refer to Analog Devices AD2S1205 Specifications and Application Notes)




Type II Position Tracking Loop Algorithm in Matlab/SIMULINK






Resolver System Simulation

Simplorer, Q3D, Maxwell, DSO, Optimetrics

Simplorer as System Simulator

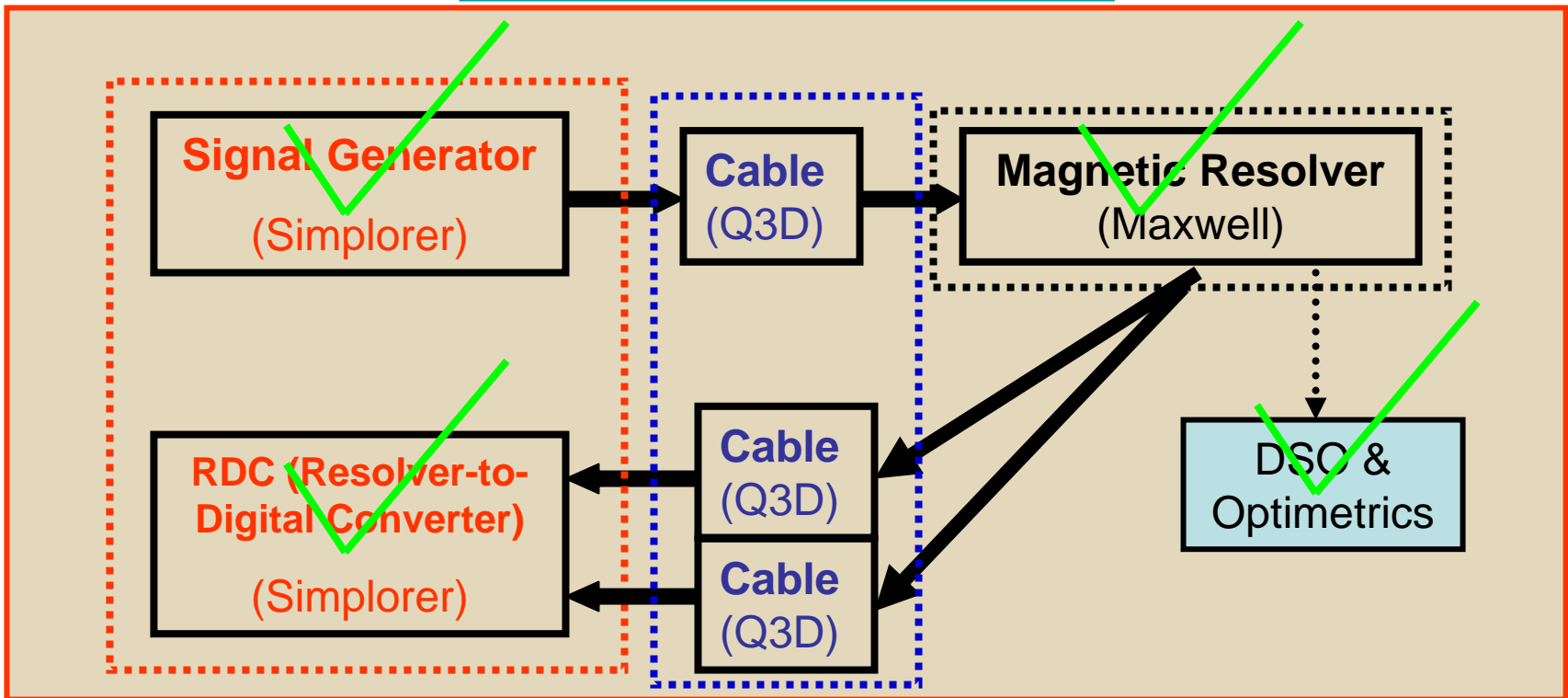

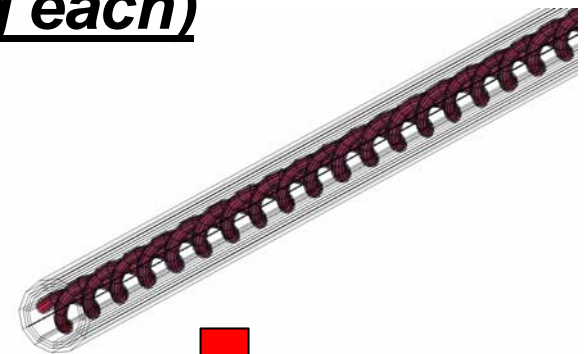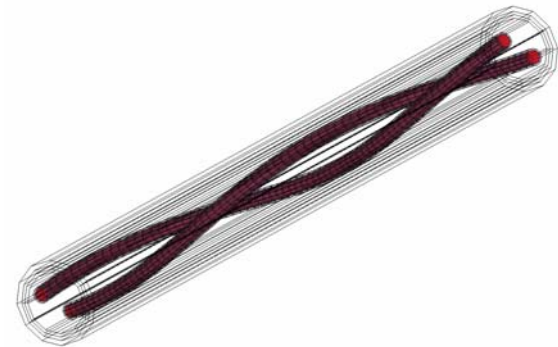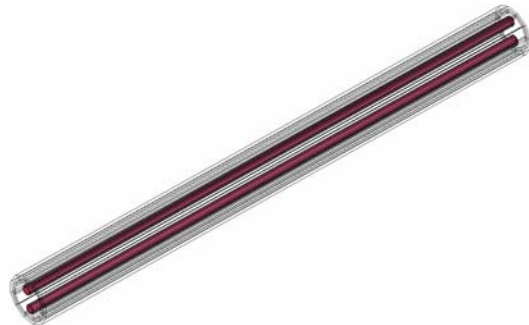Resolver Cable Paracitics Extraction (3 Cables, 1.7 meters long each)



Straight -> Twist -> Multiple Twists



Name	Value	Unit
Copper_Segment	12	
Copper_Distance	1	mm
Copper_Radius	0.2	mm
Cable_Length	Number_of_Twist/Twist_Per_Meter*1000mm	
Twist_Per_Meter	35	
Number_of_Twist	6	
Copper_Insulation	0.05	mm
Total_Length	1700	mm
Scale_Factor	Total_Length/Cable_Length/1000mm	
Cable_Insu_ID	2.2	mm
Cable_Insu_OD	2.5	mm
Cable_Shield_OD	2	mm
Cable_Shield_ID	1.8	mm

All Parameterized for Optimization

Solutions: Resolver_Cable - 3_Six_Straight

Design Variation: 'Number_of_Twist='6' Scale_Factor='9.916666666666667' Total_Length='1700mm' Twist_Per_Me

Simulation: Setup1 LastAdaptive ACP

Matrix | Convergence | Profile

Resistance Units: Ohm Matrix



Inductance Units: nH Original Export...

	Cable_Shield:Source1	Copper1:Source2	Copper2:Source3
Cable_Shield:Source1	0.0018159, 162.89	0.0018241, 161.6	0.0018298, 161.97
Copper1:Source2	0.0018241, 161.6	0.014135, 195.27	0.0034835, 163.82
Copper2:Source3	0.0018298, 161.97	0.0034835, 163.82	0.014036, 196.12


RLC Matrix



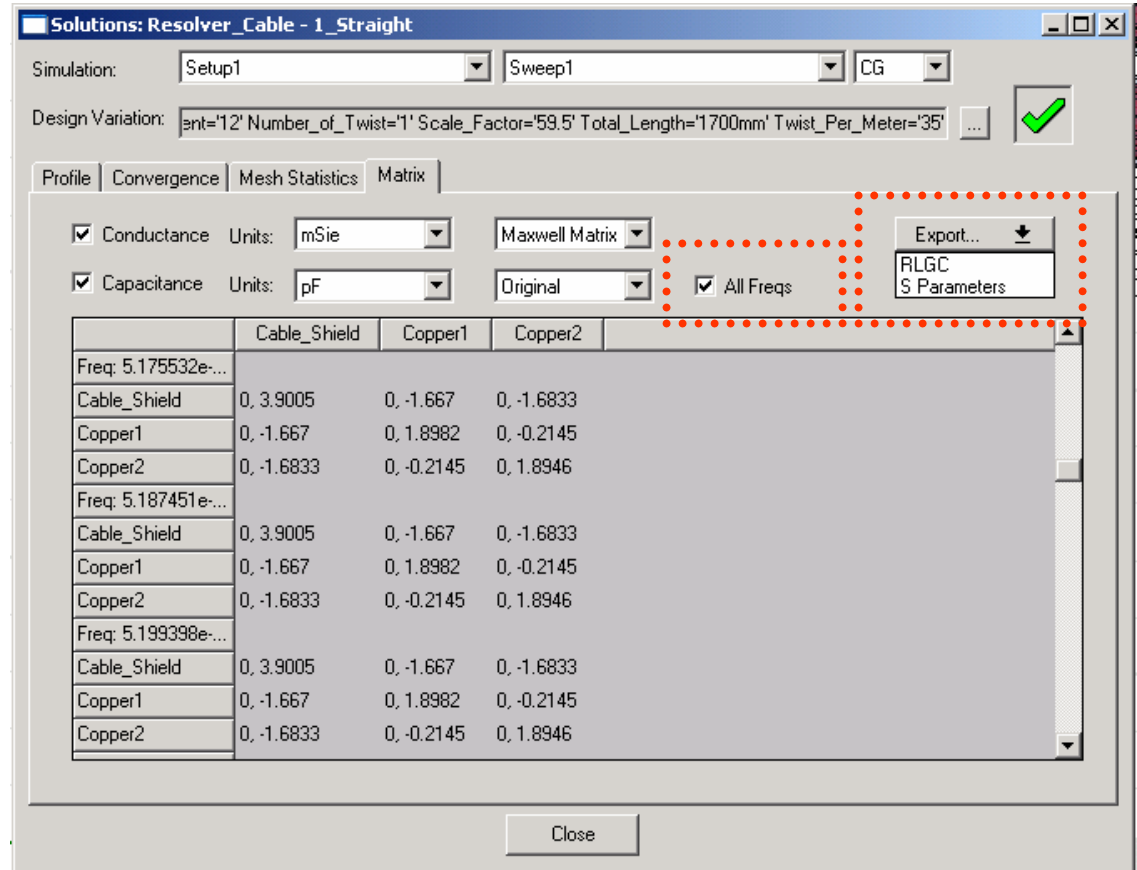
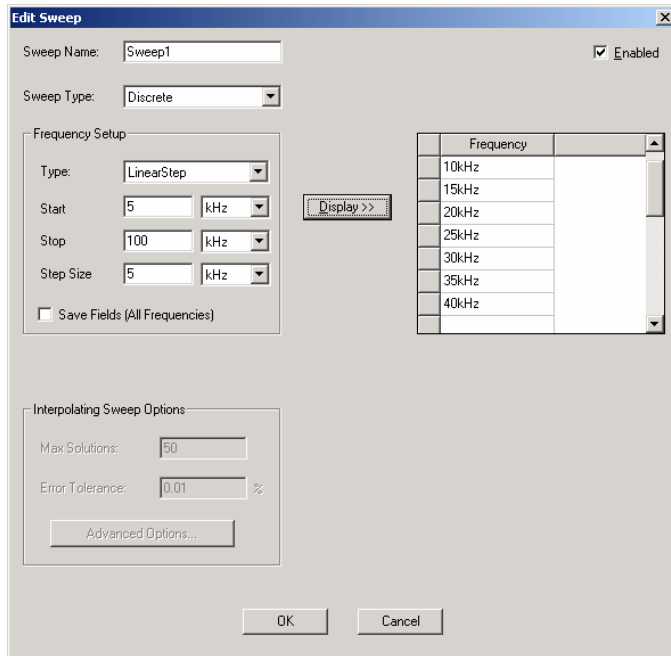
Resolver Cable Paracitics Extraction (Frequency-dependent Model Extraction)



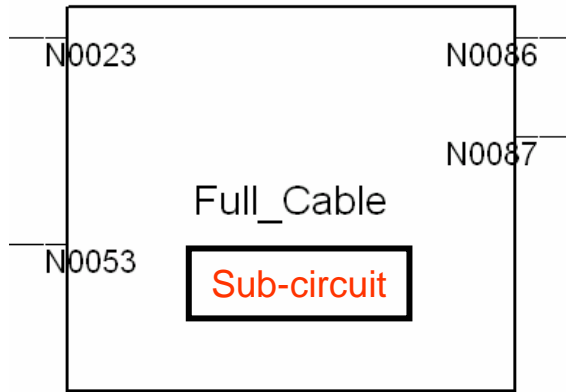Resolver Cable Paracitics Extraction (3 Cables, 1.7 meters long each)



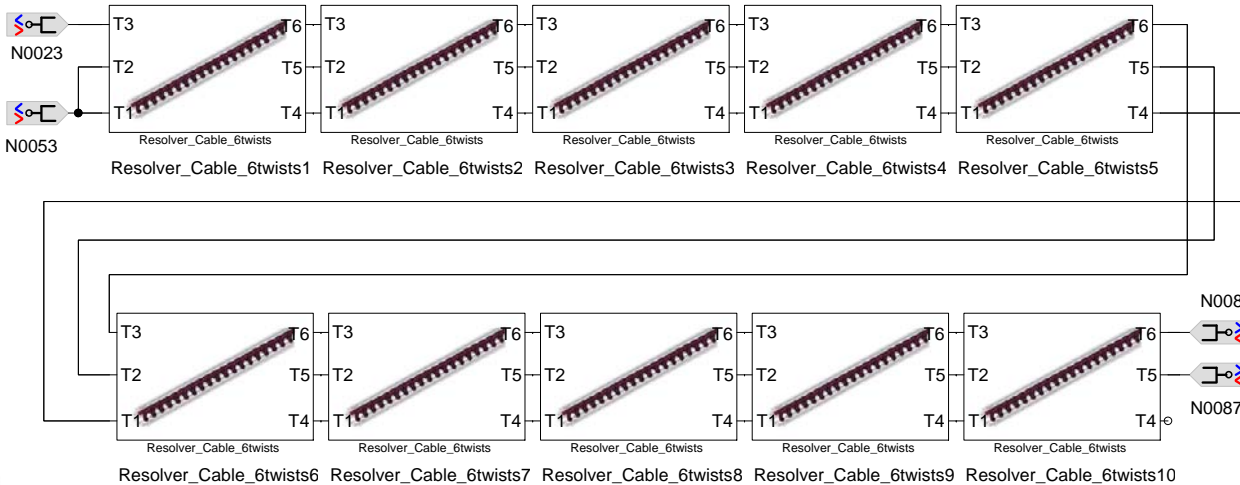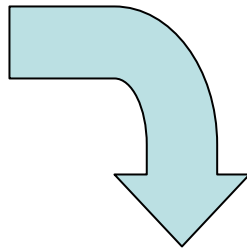Each Segment is 0.17 meters long, consists of 6 twists



```

Resolver_Cable_V8.sml
// BEGIN ANSOFT HEADER
// node T1 Cable_Shield:Source1
// node T2 Copper1:Source2
// node T3 Copper2:Source3
// node T4 Cable_Shield:Sink1
// node T5 Copper1:Sink2
// node T6 Copper2:Sink3
// Project: Resolver_Cable_V8
// Design: 1_Straight
// Format: Simplorer SHL
// Topic: Resolver_Cable_V8
// Left: T1 T2 T3
// Right: T4 T5 T6
// Creator: Ansoft Q3D Extractor 8.0
// Date: Fri Sep 07 09:26:23 2007
// Notes:
// END ANSOFT HEADER

MODELDEF Resolver_Cable_V8
(
PORT electrical: T1 ;
PORT electrical: T2 ;
PORT electrical: T3 ;
PORT electrical: T4 ;
PORT electrical: T5 ;
PORT electrical: T6 ;
MODEL Resolver_Cable_V8_half XZhalf1 TL:=T1, T2:=T2, T3:=T3, T4:=T4, T5:=T5, \
T6:=T6 ;
MODEL Resolver_Cable_V8_pariel XY TL:=T7, T2:=T8, T3:=T9 ;
MODEL Resolver_Cable_V8_half XZhalf2 TL:=T7, T2:=T8, T3:=T9, T4:=T4, T5:=T5, \
T6:=T6 ;
)

MODELDEF Resolver_Cable_V8_half
(
PORT electrical: T1 ;
PORT electrical: T2 ;
PORT electrical: T3 ;
PORT electrical: T4 ;
PORT electrical: T5 ;
PORT electrical: T6 ;
INTERM AM V1 ML:=T1, M2:=T7 ;
INTERM AM V2 ML:=T2, M2:=T8 ;
INTERM AM V3 ML:=T3, M2:=T9 ;
INTERM R R1 ML:=T7, M2:=T10 ( R:=0.00080659048 ) ;
INTERM R R2 ML:=T8, M2:=T11 ( R:=0.0021563799 ) ;
INTERM R R3 ML:=T9, M2:=T12 ( R:=0.0021563799 ) ;
INTERM I I1_1 ML:=T10, M2:=T7 ( QUANT:=V2.I, FACT:=0.179727 ) ;
INTERM I I1_2 ML:=T10, M2:=T7 ( QUANT:=V3.I, FACT:=0.179191 ) ;
INTERM I I2_1 ML:=T11, M2:=T8 ( QUANT:=V2.I, FACT:=0.0452452 ) ;
INTERM I I2_2 ML:=T11, M2:=T8 ( QUANT:=V3.I, FACT:=0.0427265 ) ;
INTERM I I3_1 ML:=T12, M2:=T9 ( QUANT:=V2.I, FACT:=0.0451936 ) ;
INTERM I I3_2 ML:=T12, M2:=T9 ( QUANT:=V3.I, FACT:=0.0426927 ) ;
INTERM L L1 ML:=T10, M2:=T4 ( L:=0.514693e-009 ) ;
INTERM L L2 ML:=T11, M2:=T5 ( L:=1.162079e-009 ) ;
INTERM L L3 ML:=T12, M2:=T6 ( L:=1.1608523e-008 ) ;
INTERM M M1_1 ( LL:=L1.L, L2:=L2.L, K:=0.858496 ) ;
INTERM M M1_2 ( LL:=L1.L, L2:=L3.L, K:=0.859014 ) ;
INTERM M M2_1 ( LL:=L2.L, L2:=L3.L, K:=0.752119 ) ;
)

MODELDEF Resolver_Cable_V8_pariel
(
PORT electrical: T1 ;
PORT electrical: T2 ;
PORT electrical: T3 ;
INTERM C C1_0 ML:=T1, M2:=GND ( C:=5.4236151e-013 ) ;
INTERM C C1_1 ML:=T1, M2:=T2 ( C:=1.6489764e-011 ) ;
INTERM C C1_2 ML:=T1, M2:=T3 ( C:=1.6540195e-011 ) ;
INTERM C C2_0 ML:=T2, M2:=GND ( C:=9.7627146e-015 ) ;
INTERM C C2_1 ML:=T2, M2:=T3 ( C:=2.1497155e-012 ) ;
INTERM C C2_2 ML:=T2, M2:=GND ( C:=2.9842619e-015 ) ;
)


```



Resolver System Simulation

Simplorer, Q3D, Maxwell, DSO, Optimetrics

Simplorer as System Simulator

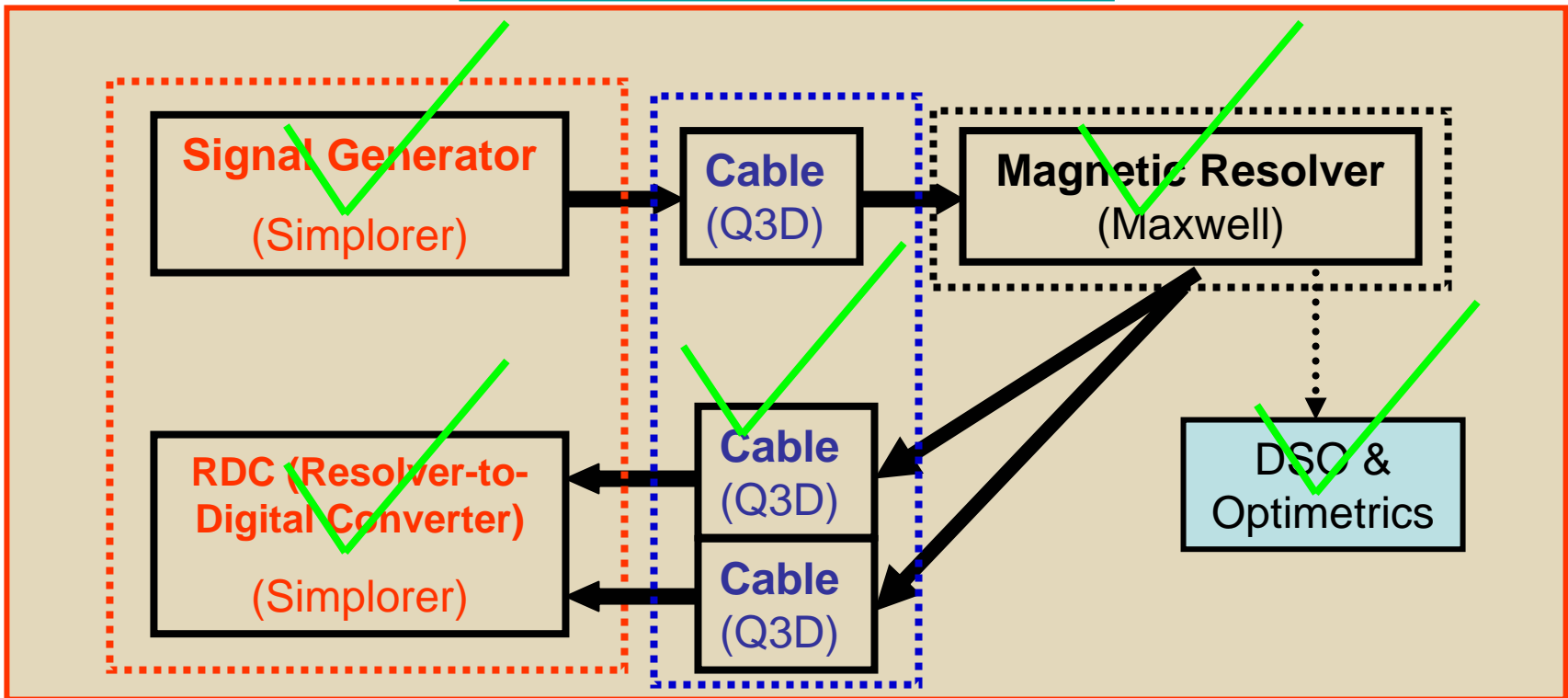

Resolver Behavioral Model

Initialization

EQU

Input_AC_Mag := 1

Input_AC_Freq:=12k

Conductor_Ratio:=0.1

Number_of_Rotor_Poles :=

Rotor_Speed :=100

Rotor_Position := Rotor_Speed *(360/60) * t

Tend := 45/(Rotor_Speed*(360/60))

Hmin := 1/Input_AC_Freq/100

Hmax := Hmir

Excitator

EQU

Vin := Input_AC_Mag * sin(2*PI*Input_AC_Freq*t)

Resolver_Output

EQU

Vout_sin := Conductor_Ratio * sin(Number_of_Rotor_Poles*Rotor_Position*(PI/180))*V



Vout_cos := Conductor_Ratio * cos(Number_of_Rotor_Poles*Rotor_Position*(PI/180))*V

$$V_{excitation} = U1 * \sin(2 * \pi * Freq * t)$$

$$V_{Out_Sin} = U2 * \sin(2 * \pi * Freq * t) * \sin(\theta)$$

$$V_{Out_Cos} = U2 * \sin(2 * \pi * Freq * t) * \cos(\theta)$$

Resolver

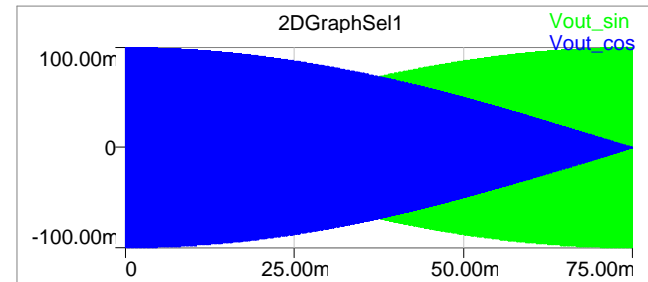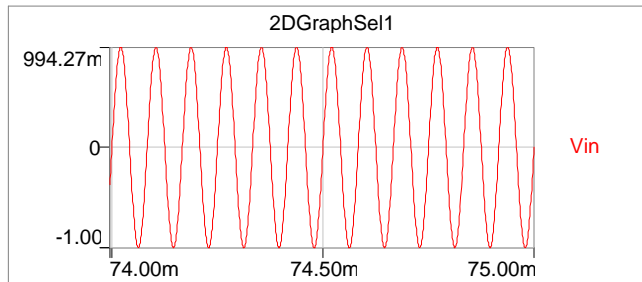

Resolver and RDC Model

Initialization

EQU

Input_AC_Mag := 1
 Input_AC_Freq:=12k
 Conductor_Ratio:=0.1
 Number_of_Rotor_Poles :=;
 Rotor_Speed :=10C
 Rotor_Position := Rotor_Speed *(360/60) * t
 Tend := 45/(Rotor_Speed*(360/60))
 Hmin := 1/Input_AC_Freq/100
 Hmax := Hminr


Excitation

EQU


Vin := Input_AC_Mag * sin(2*PI*Input_AC_Freq*t)
 Resolver_Output
EQU

Vout_sin := Conductor_Ratio * sin(Number_of_Rotor_Poles*Rotor_Position*(PI/180))*Vin
 Vout_cos := Conductor_Ratio * cos(Number_of_Rotor_Poles*Rotor_Position*(PI/180))*Vinr

Resolver

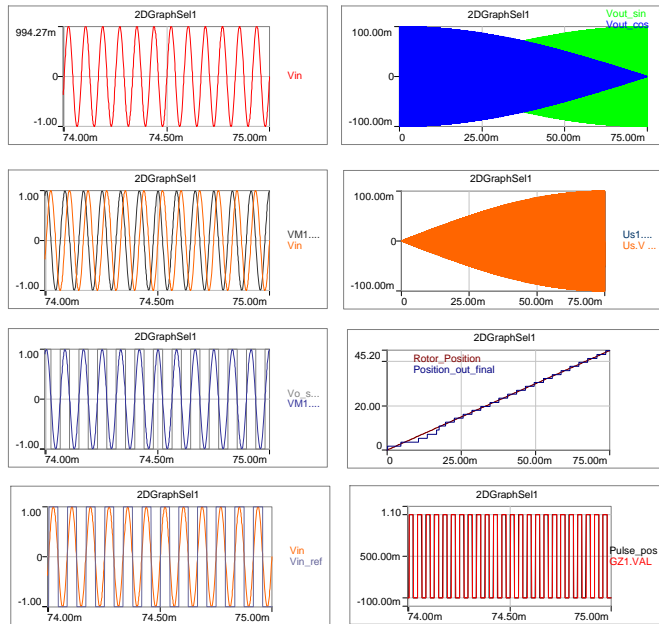



Resolver and RDC Behavioral Model

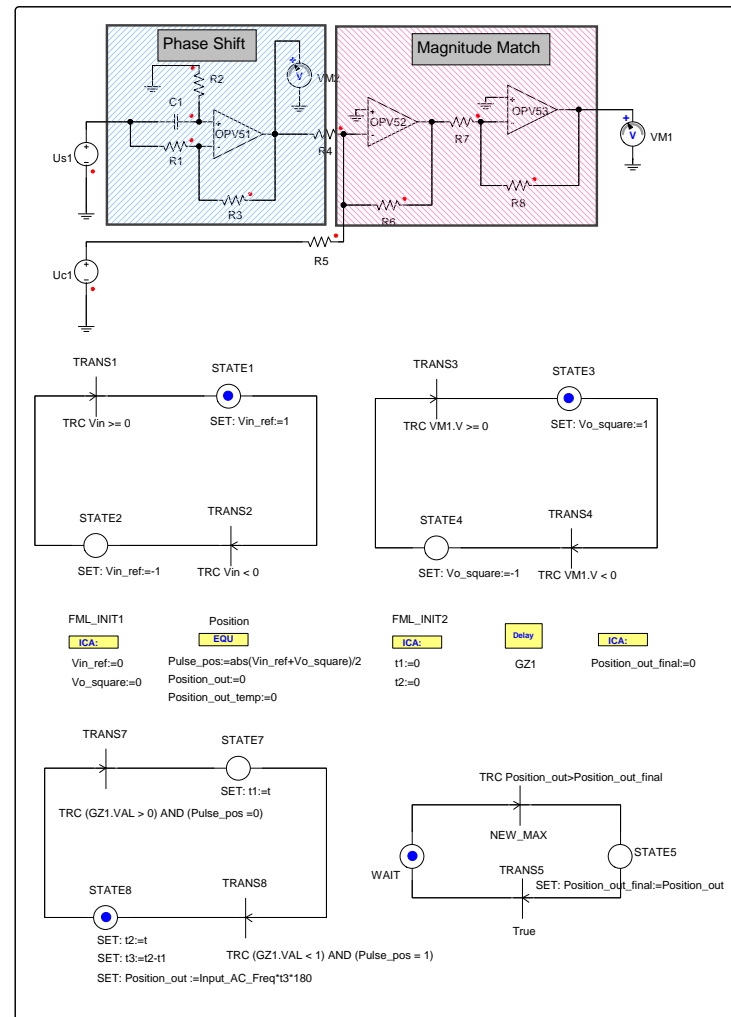

Classical RDC (Resolver-to-Digital Convertor)





Position Output Accuracy

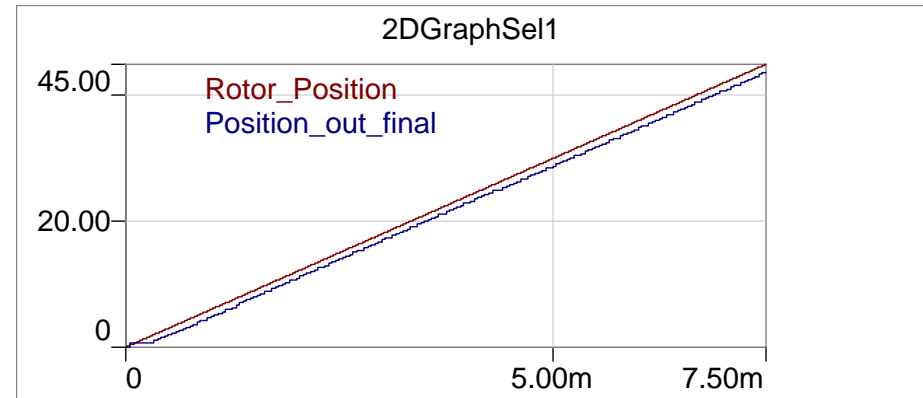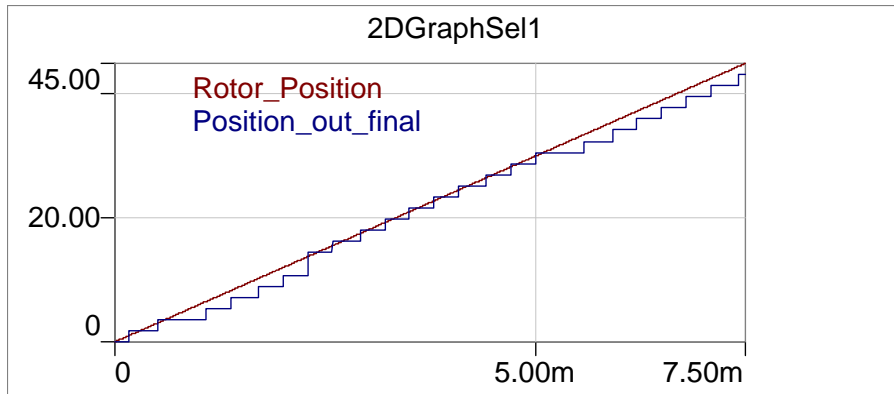

12k Hz excitation, 1,000RPM speed, 0.1us sampling time

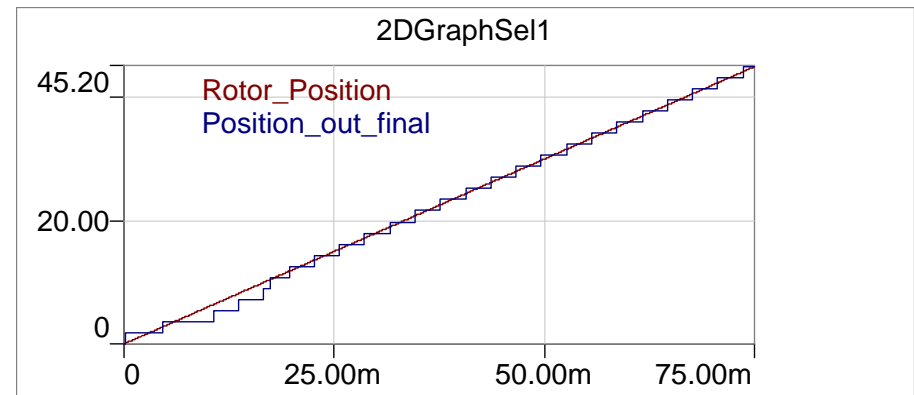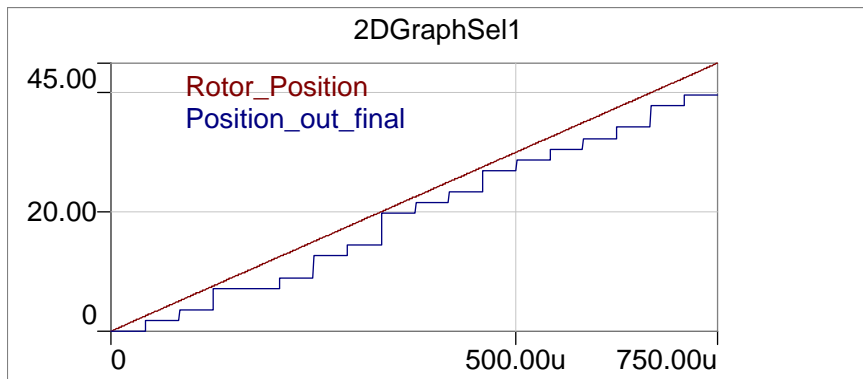12k Hz excitation, 1,000RPM speed, 0.01us sampling time







12k Hz excitation, 10,000RPM speed, 0.1us sampling time


12k Hz excitation, 100RPM speed, 0.1us sampling time



Resolver System Integration

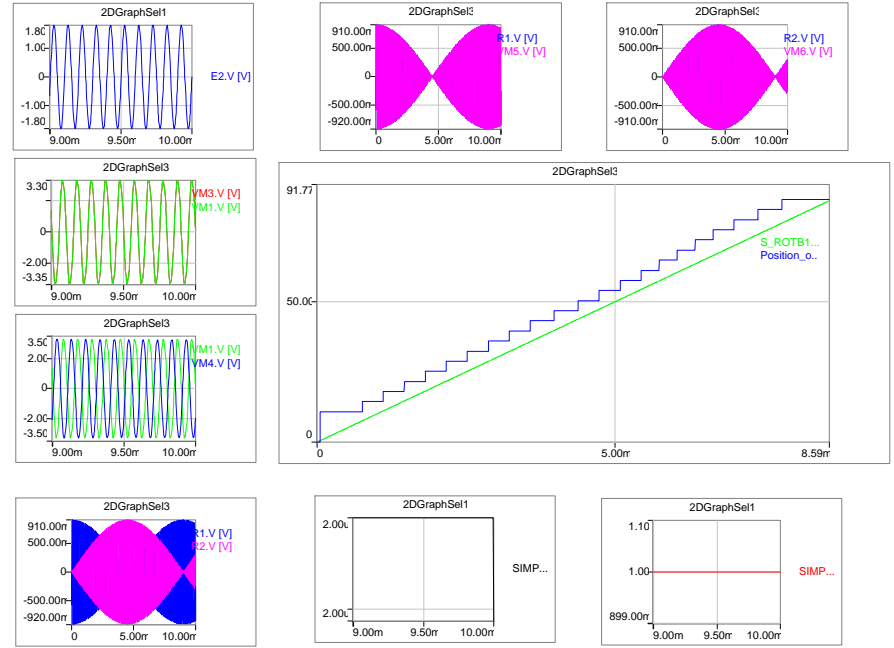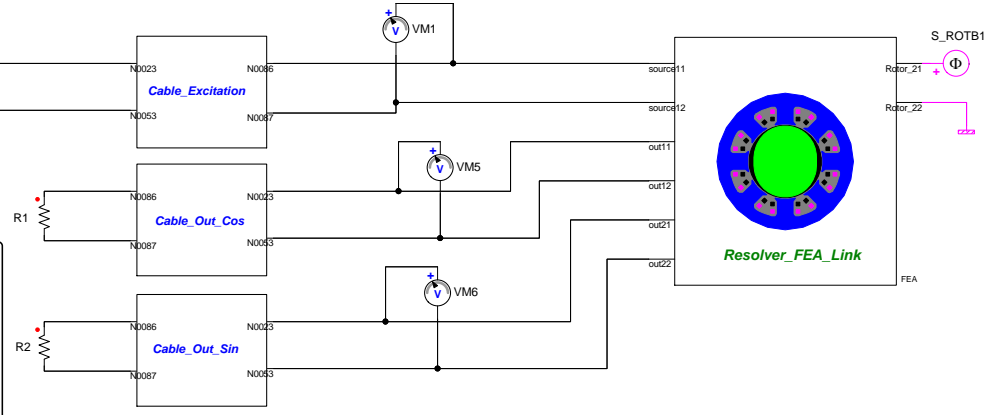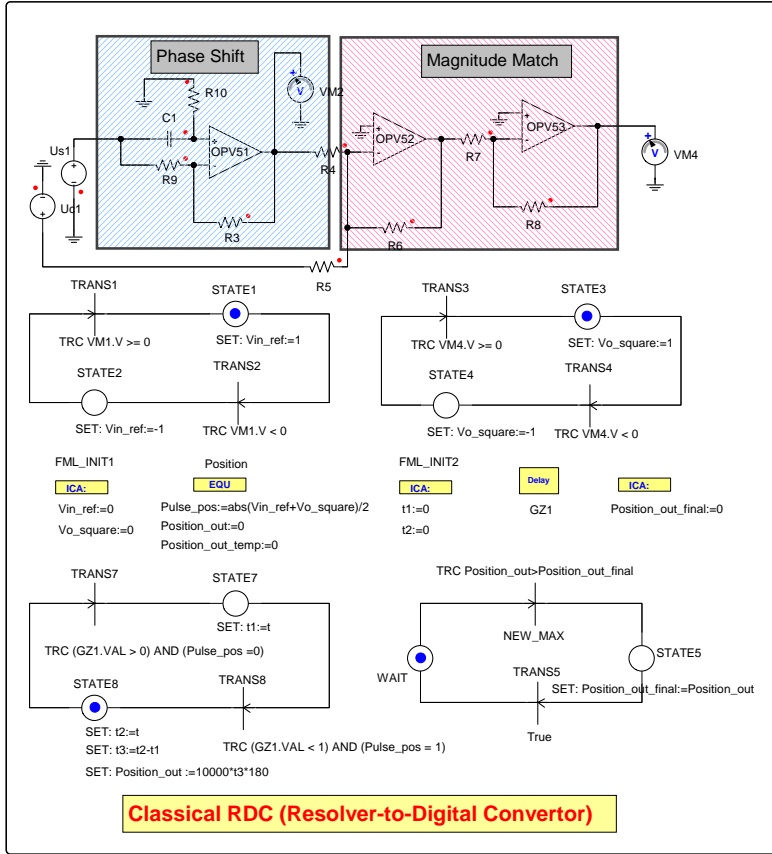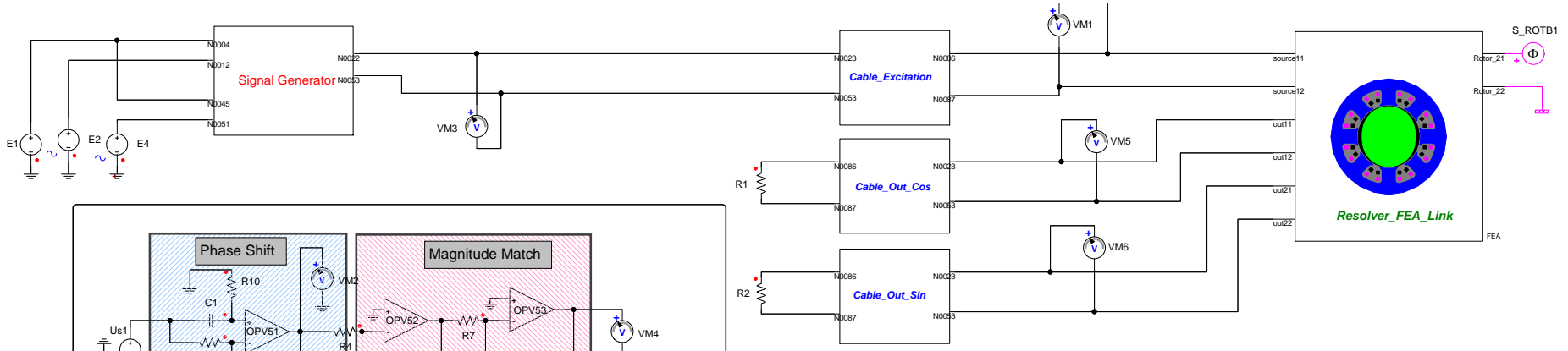

Resolver System Integration

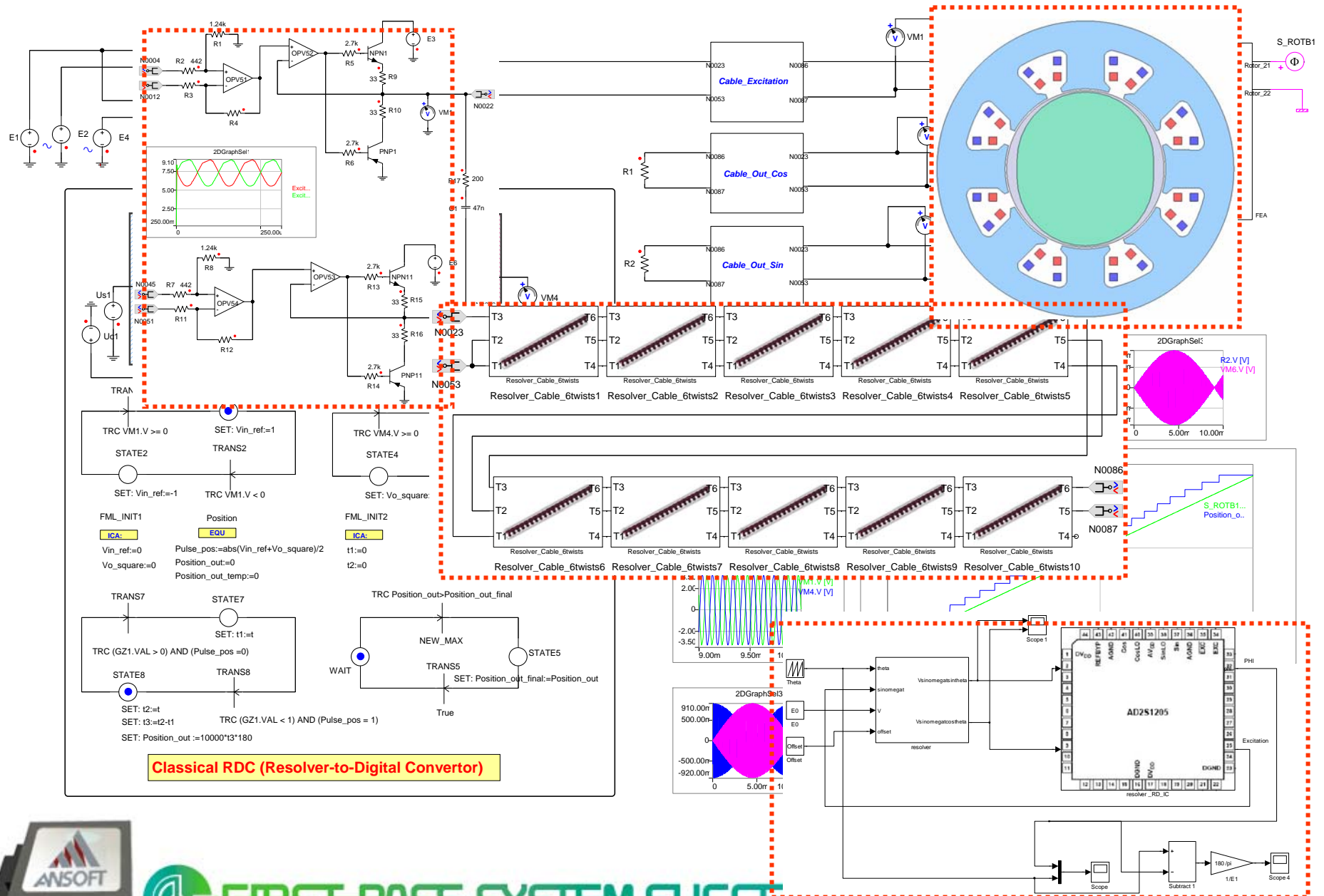

Classical RDC (Resolver-to-Digital Converter)







Conclusions

- Resolver Deserves More Attention for Applications where Rugged, High-accuracy Position Sensing is Needed
- A Systematic Approach is Necessary for Signal Generator / Resolver / Cable / Resolver-to-Digital Converter System Optimization
- Simplorer as a Multi-level / Multi-domain System Simulator is an Ideal Tool for Applications where Electric Circuitry, Field Simulation and Parasitics are Involved
- Each Tool (Simplorer / Maxwell / Q3D) can be Used as a Stand-alone Design Tool to Optimize Components (Signal Generator / RDC Algorithm / Resolver / Cable) in the System
- This Systematic Approach Ensures Engineers from both Sides of Component Design / System Integration to be Successful



Future Work:

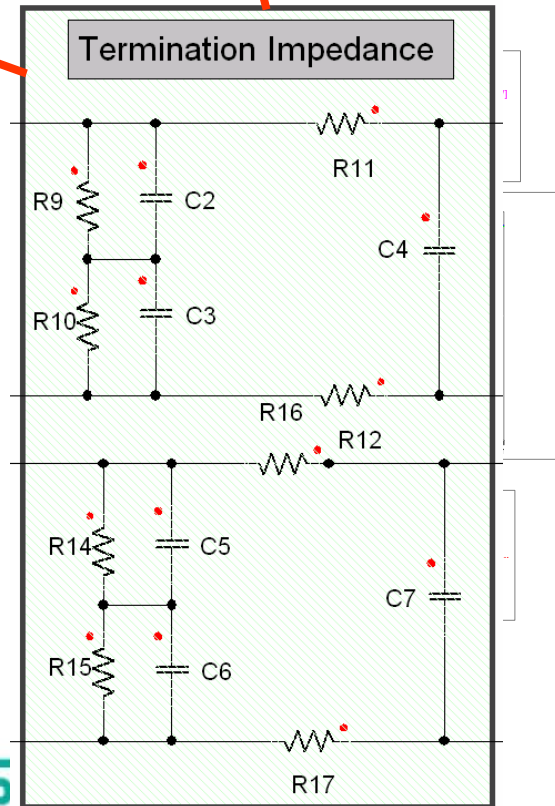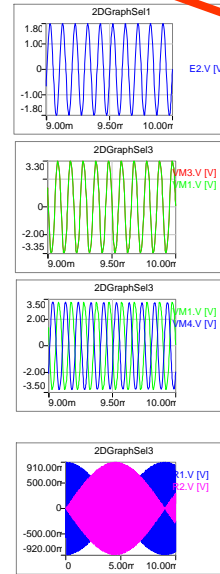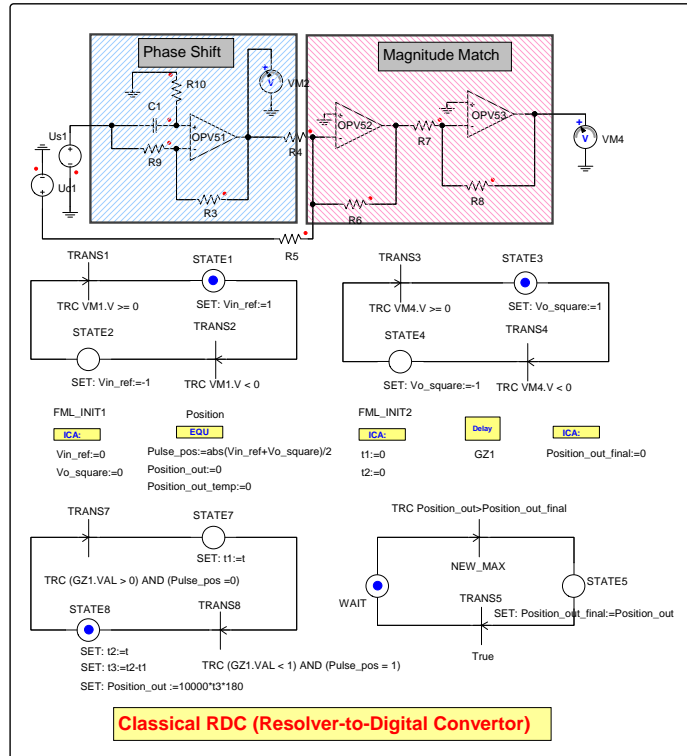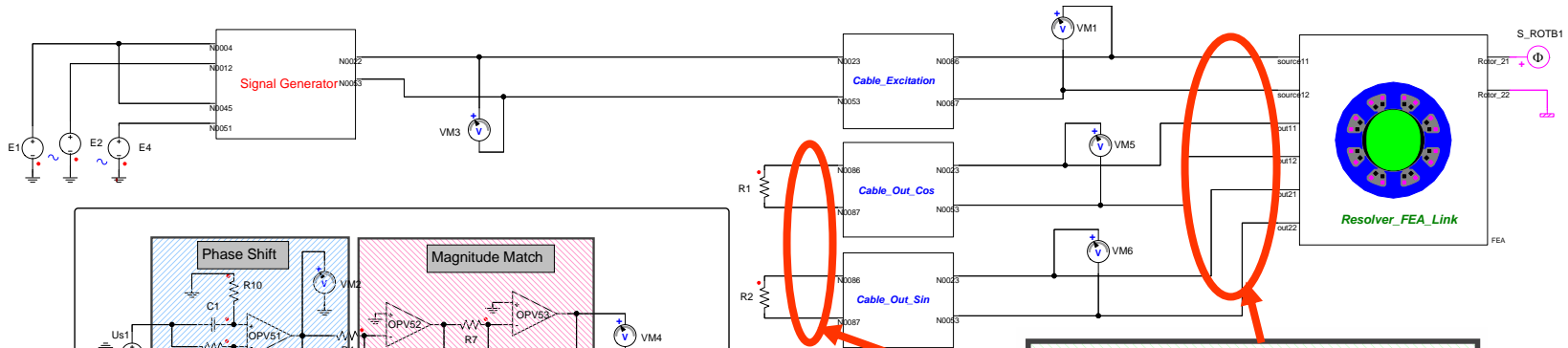1. Add Termination Impedance, to take into account the harmonics and transmission line reflection



Future Work:

2. Replace the classical RDC with Type II Position Tracking mode

