

Part I:
Design of High Frequency
VCO and Divider
in CMOS Technologies

Wen-Chieh (Steven) Wang
Department of Electronics Engineering
National Chiao-Tung University

Outlines

■ Introduction

■ Circuit Design Example

- Case I: High Frequency VCO and Divider
- Case II: Wide Tuning Range VCO for UWB

■ Conclusions

Introduction

- In RFIC design, circuits are sensitive to parasitic, including parasitic capacitors and inductors.
- The Ansoft HFSS helps consider and extract these parasitic effect. Besides, the EM coupling effect can also be figured out.
- The Ansoft Designer/Nexxim is a powerful simulator that can handle larger amount transistors and have shorter simulation times.
- Two case studies using Ansoft tools including Designer/Nexxim and HFSS are discussed in this presentation.



Case I : High Frequency VCO and Divider

■ Circuit of VCO (single-ended)

- By simple calculation,

$$i_{in1} = a_1 + jb_1; \quad i_{in2} = \alpha [a_{gm} + jb_{gm}]$$

- The negative-R results from $\alpha \cdot a_{gm}$
- Z_D should be designed such that $a_1 > 0$
- It is easy to prove that $\underline{Z_D}$ **should be inductive** and the resonated frequency of Z_D and C_{GD} should be smaller than the VCO oscillating frequency

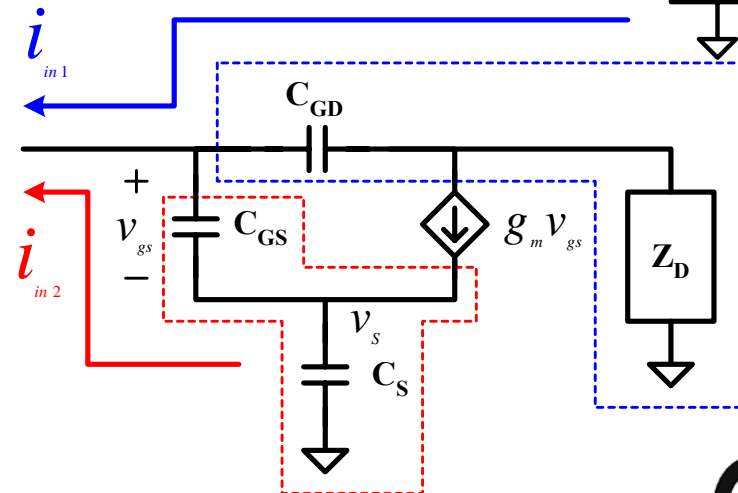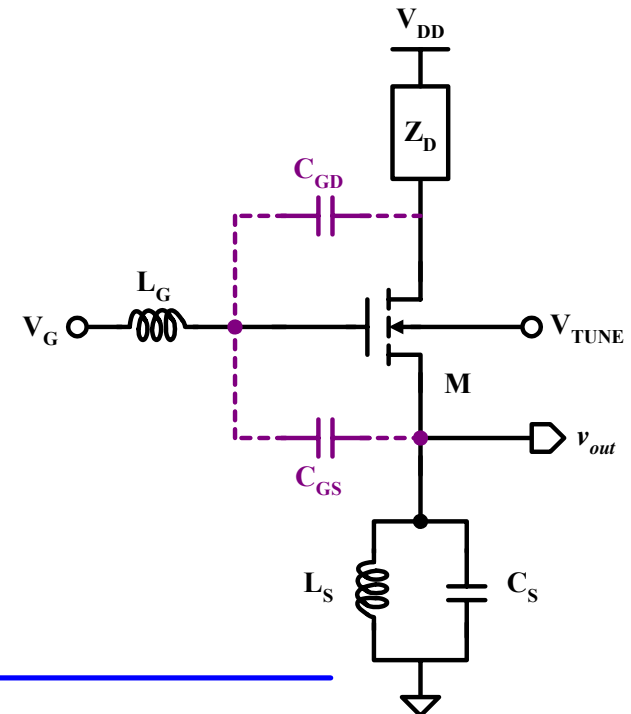

Case I : High Frequency VCO and Divider


■ Noise consideration

● The general model for a VCO

- $\langle v_n^2 \rangle \approx kT/C_P = kT\omega_0^2 L_P$
- V_{tank} is ratio to R_P

● Design guide of the LC tank

- Minimizing the value of L_P
- Minimizing the value of R_P
- Designing the value of L_P/R_P^2 as small as possible

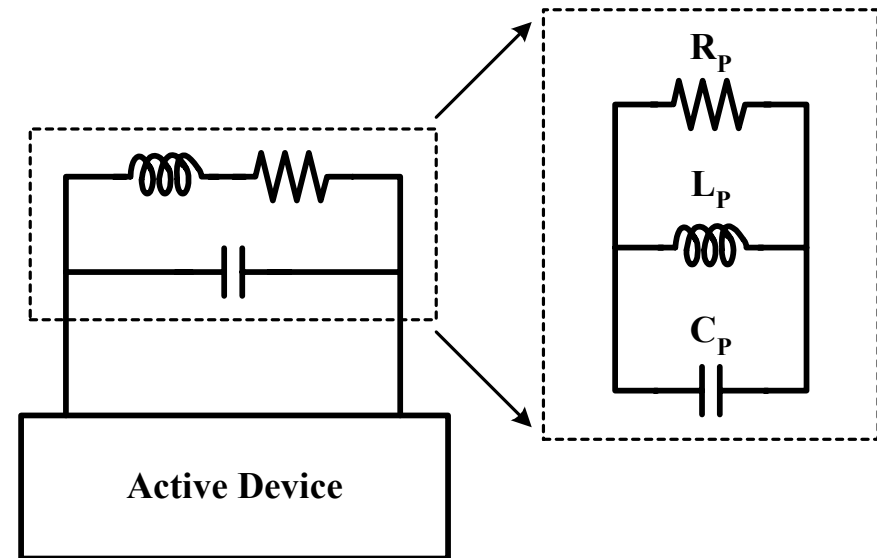

Case I : High Frequency VCO and Divider

■ Consideration of the single-ended VCO

- 3 ac ground in the circuit

➤ V_{DD} , V_G , V_{TUNE}


- It is difficult to design idea ac ground in high frequency

■ Differential type of VCO

- Differential circuit structure is needed to prevent such ac ground node.


Case I : High Frequency VCO and Divider

■ Injection locked frequency divider

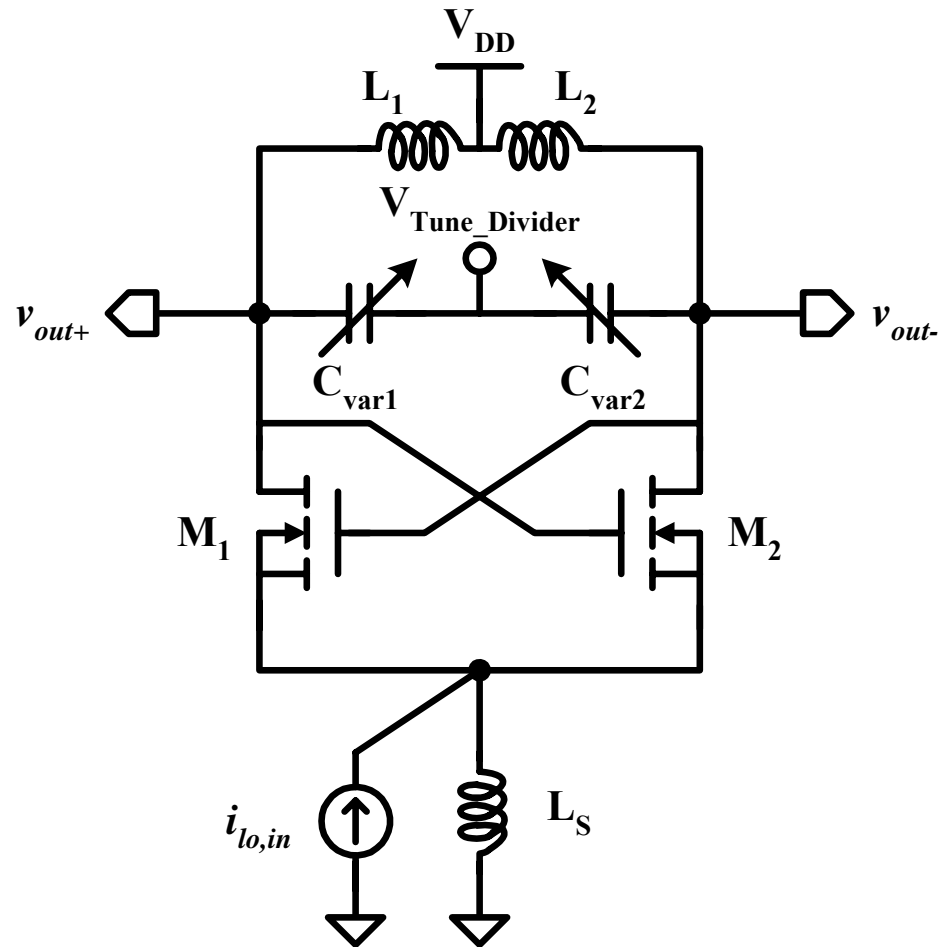


Case I : High Frequency VCO and Divider

■ Whole circuit of VCO and Divider

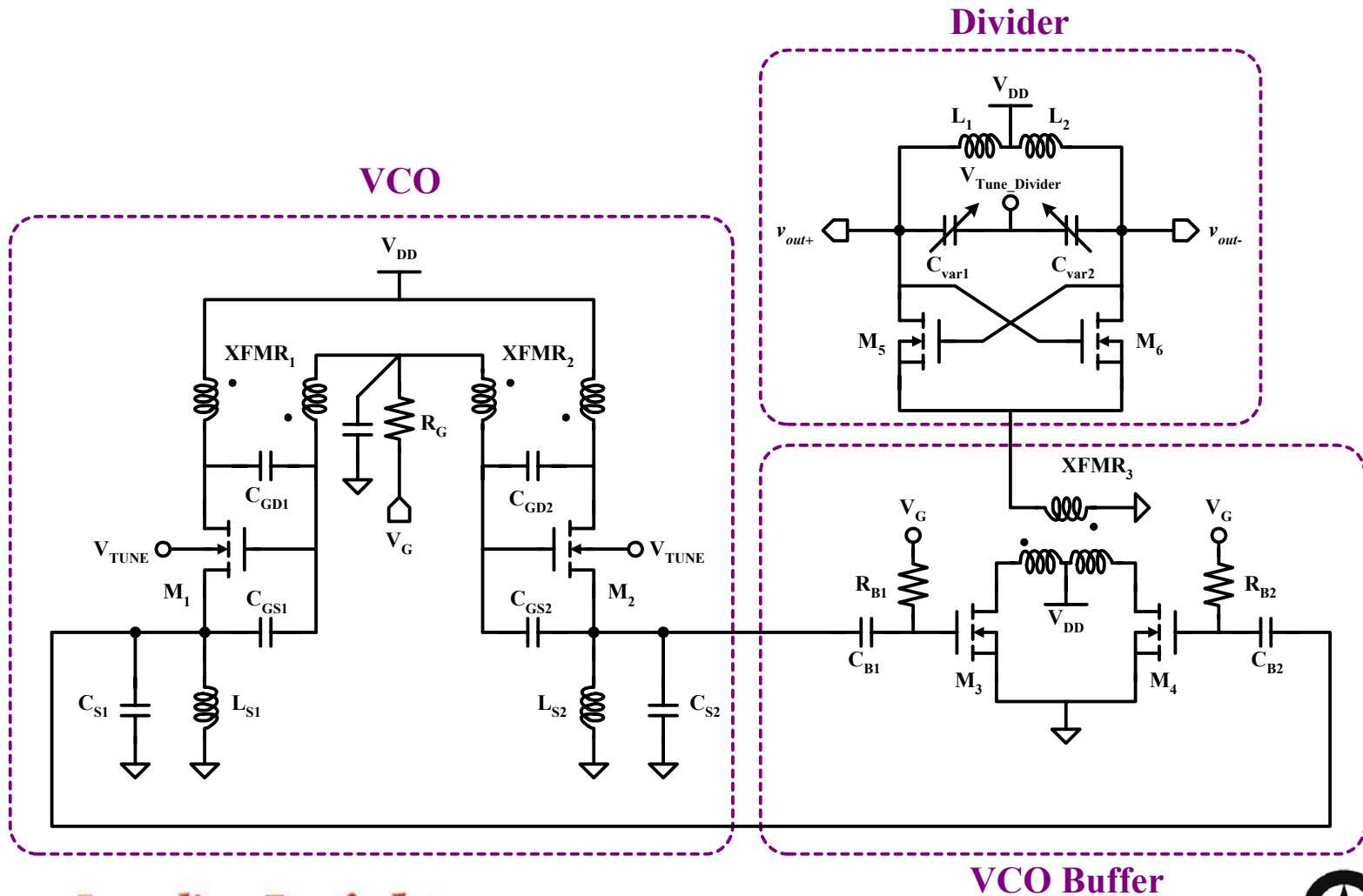

Case I : High Frequency VCO and Divider

Layout Diagram of VCO in HFSS 3-D view

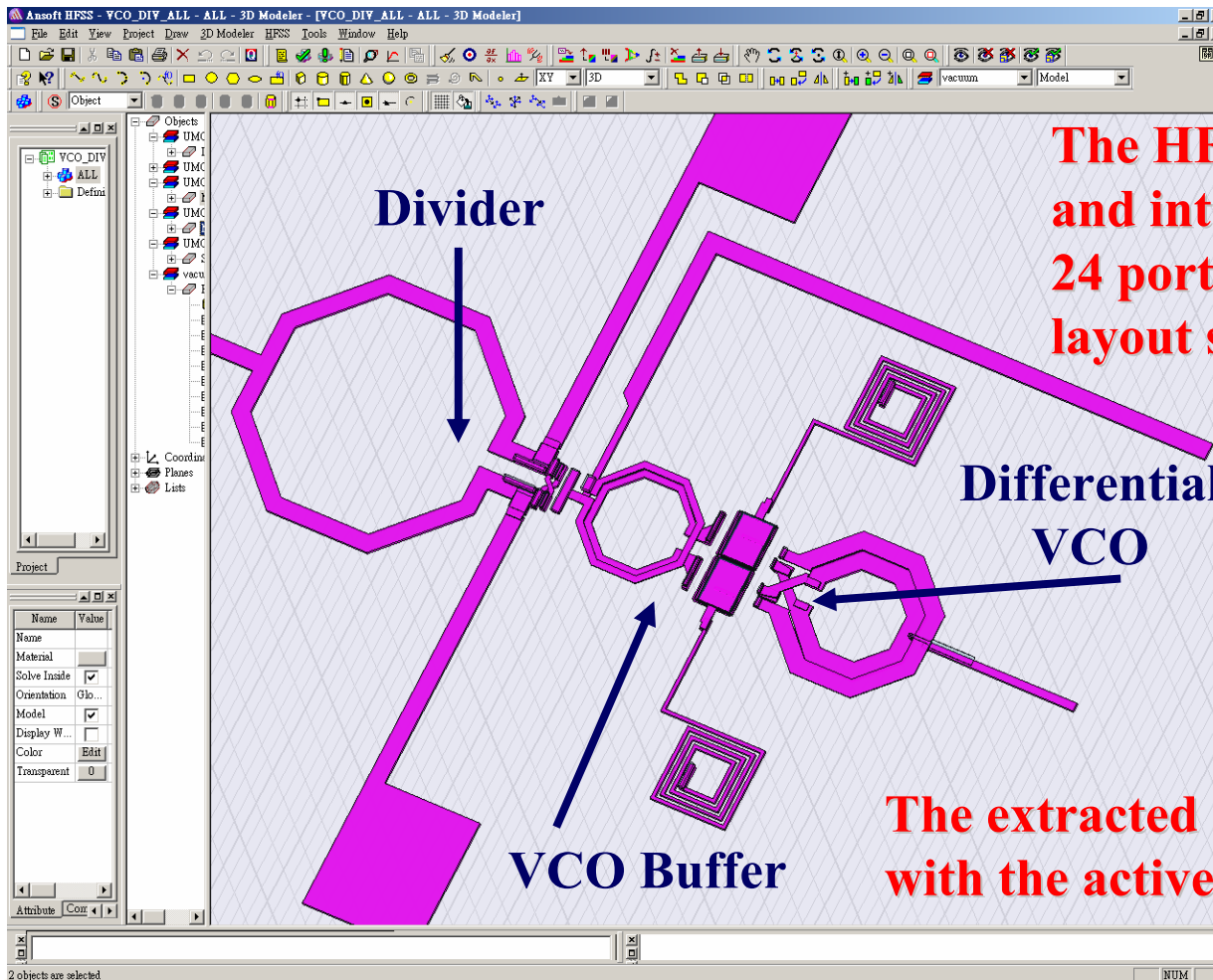


The HFSS extracts the parasitic and interconnection effect. 24 ports are considered in this layout structure

The extracted SNP file is co-simulated with the active devices by Ansoft Nexxim


Case I : High Frequency VCO and Divider

■ Simulation results – (1) VCO

Characteristics of negative-R

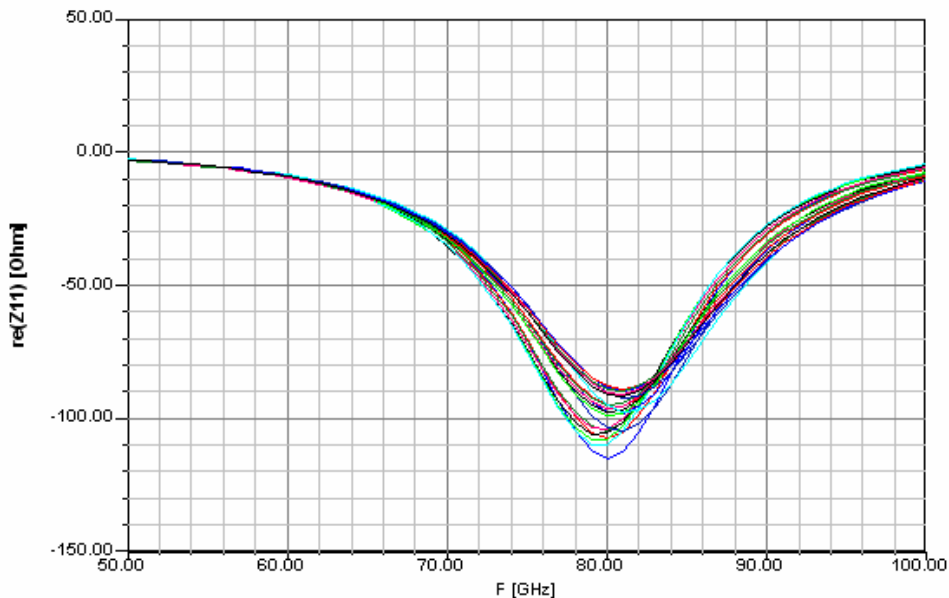


Tuning Range From 79.4GHz to 81.4 GHz

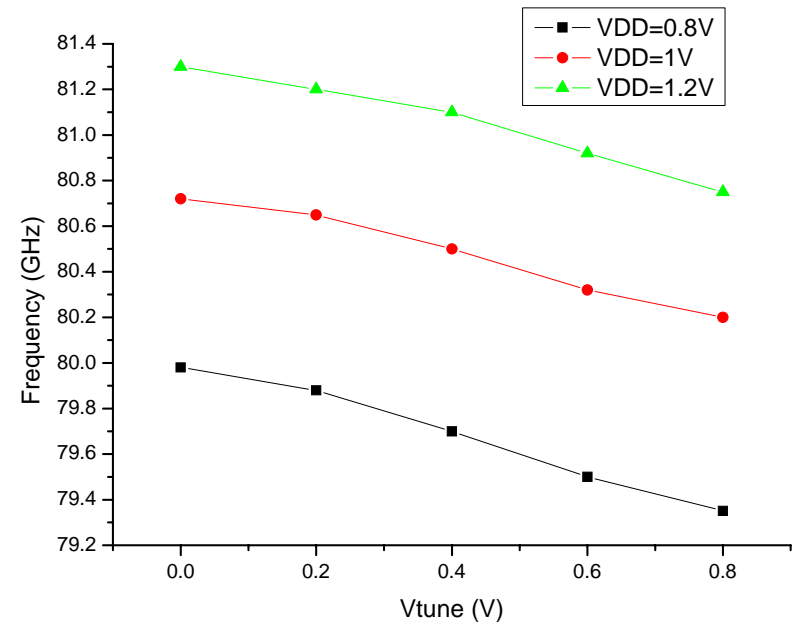

Case I : High Frequency VCO and Divider

■ Simulation results – (2) VCO

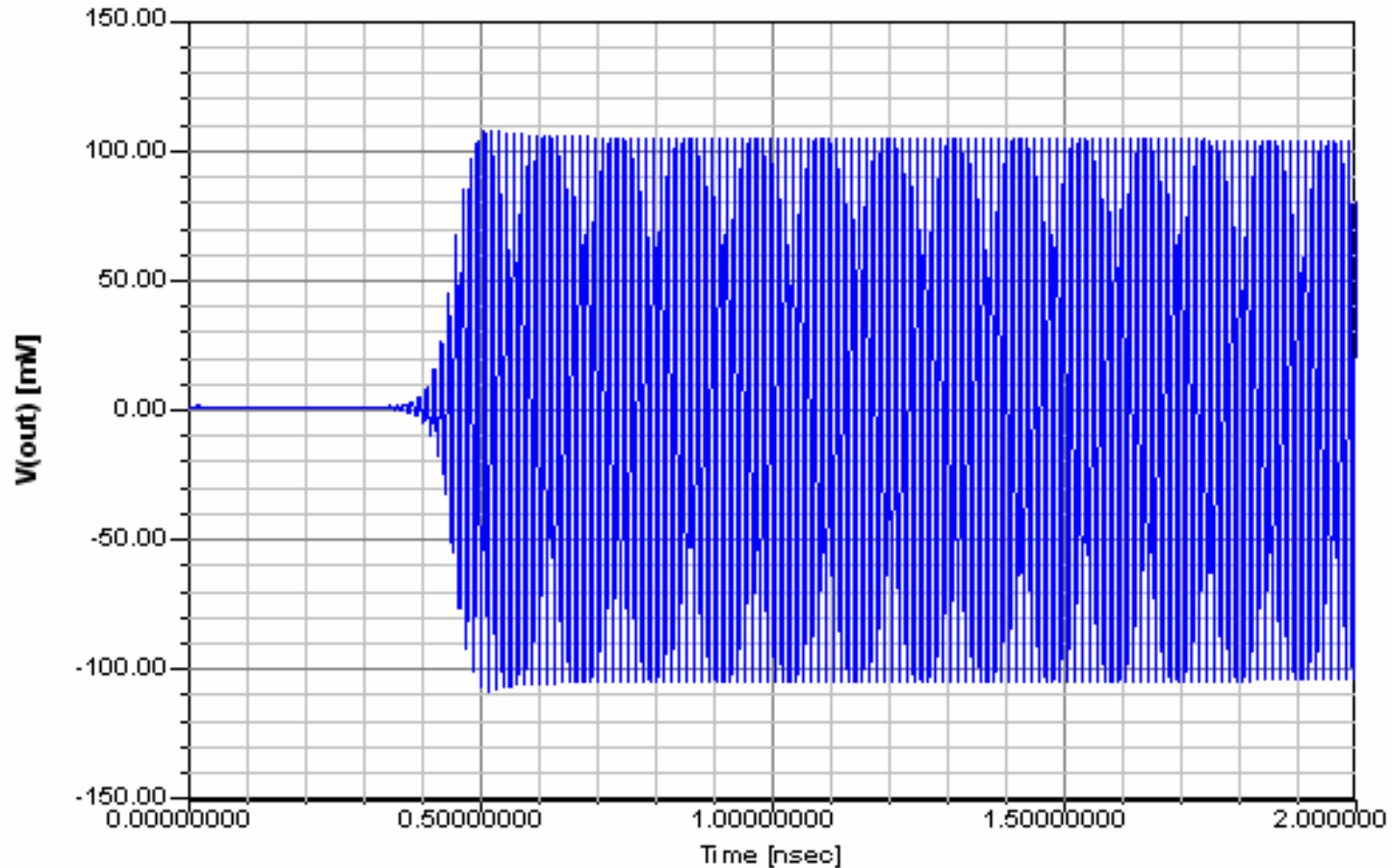


Case II : Wide Tuning Range VCO for UWB

■ Wide tuning range LC tank

● Half-turn inductor

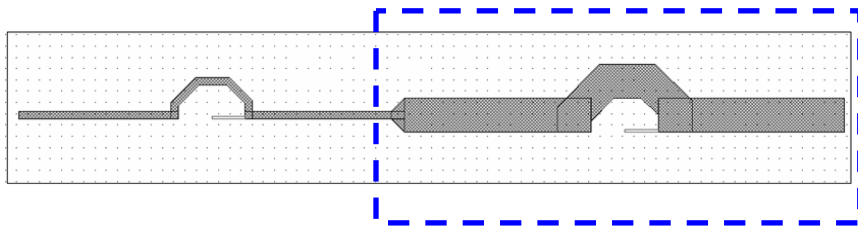
- Inductance decreases before its self-resonate frequency. This characteristic can be used to increase the tuning range of VCO.



Wider metal width has higher Q but larger parasitic capacitance that decrease the tuning range.

Therefore, 2 half-turn inductors are in series.


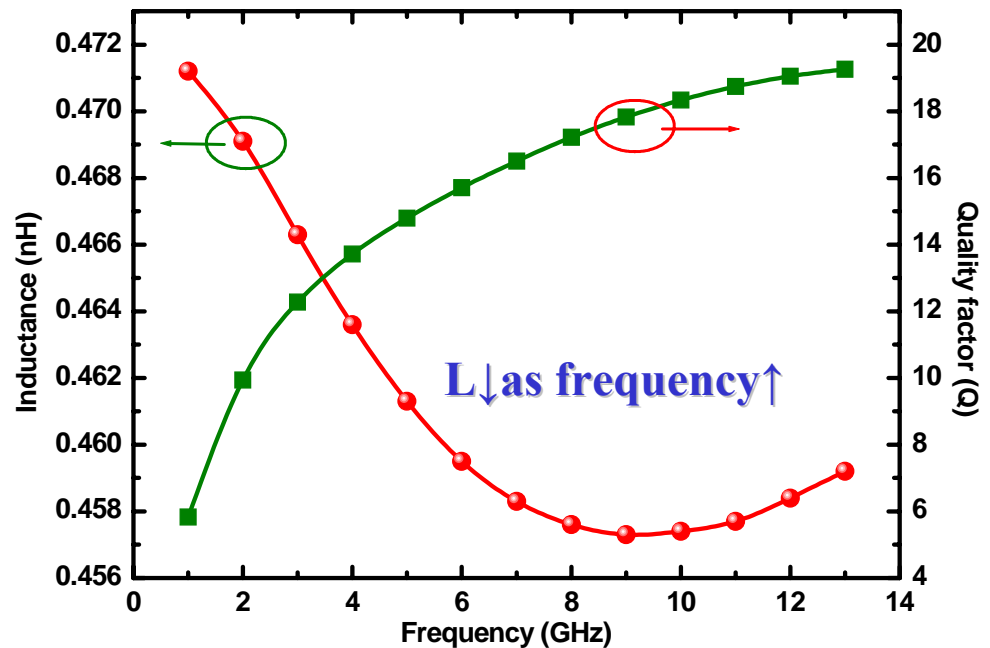
The 2nd one is chosen wider metal to increase Q slightly.



Wide Tuning Range VCO for UWB

■ Wide tuning range LC tank

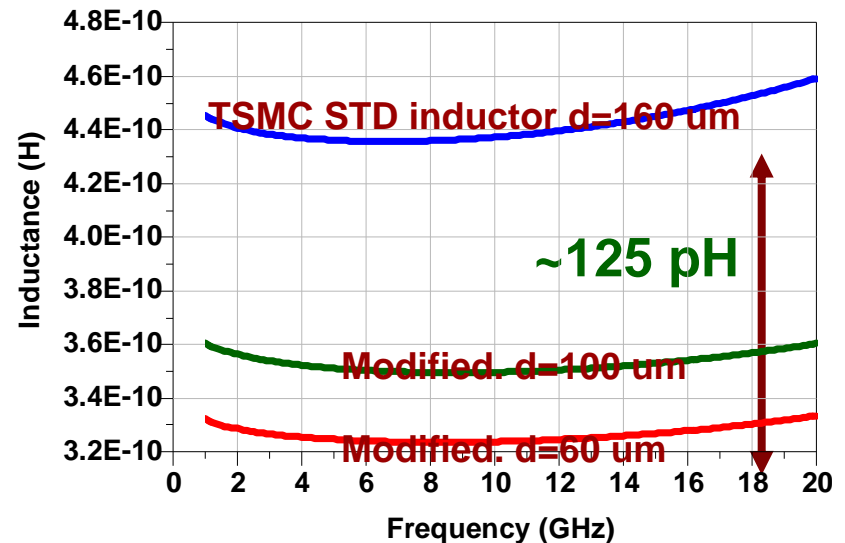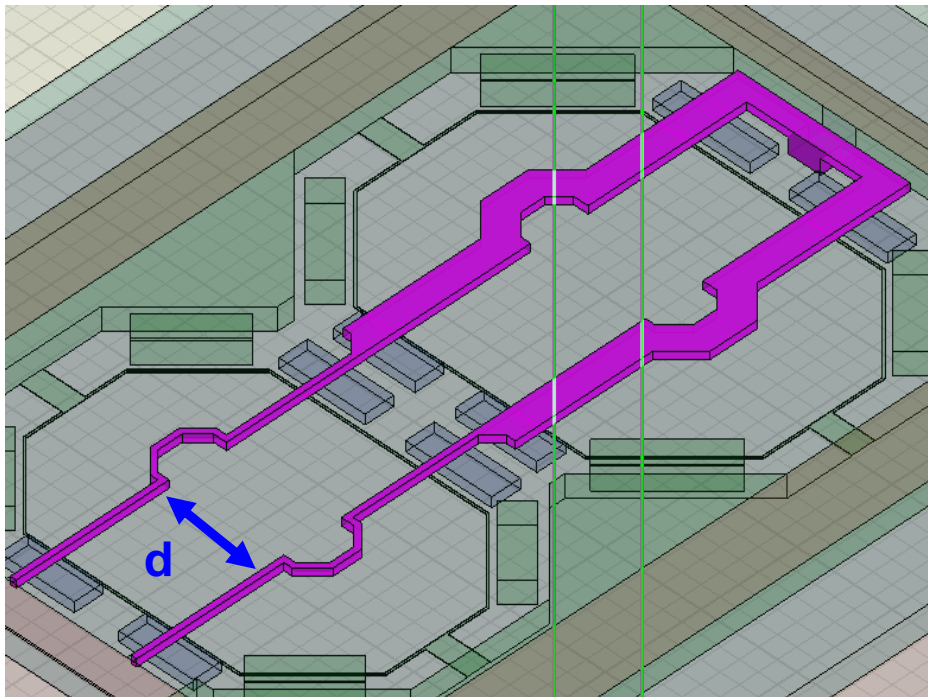- The half-turn inductors in series are slightly modified from the device provided by foundry to reduce active area . The HFSS is adopted to verify the inductors.





$L \downarrow$ as frequency \uparrow
at the frequency below 10 GHz

Case II : Wide Tuning Range VCO for UWB

Wide tuning range LC tank

- More group number reduce gate resistance that increase Q_{var} .
- Gate is connected to VCO output and S/D are connected bias (ac ground point). This can result in wider tuning range and better phase noise.


- $Q_{\text{var}} \propto L^{-2}$. Tuning capability: $(C_{\text{max}} / C_{\text{min}}) \propto (L / L_{\text{min}})$

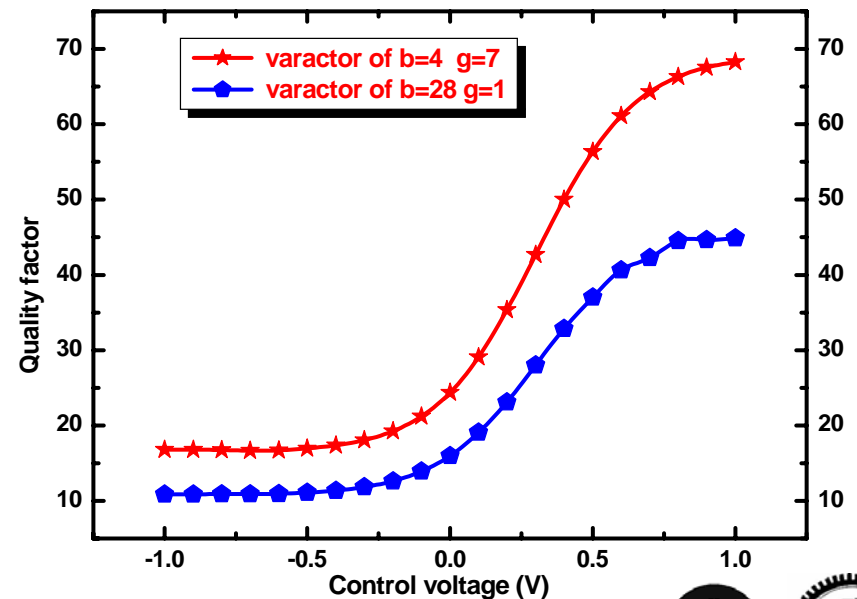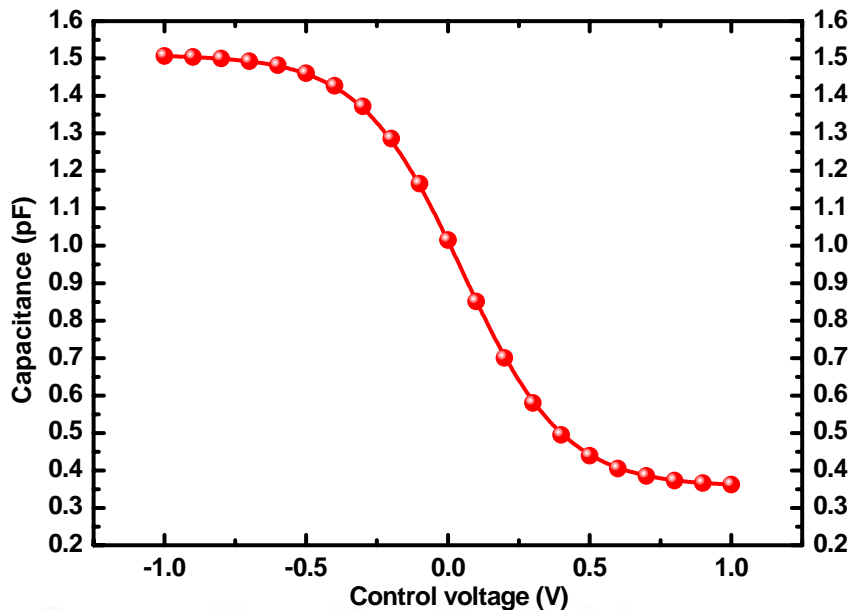

Case II : Wide Tuning Range VCO for UWB

■ Circuit of the wide tuning range quadrature VCO

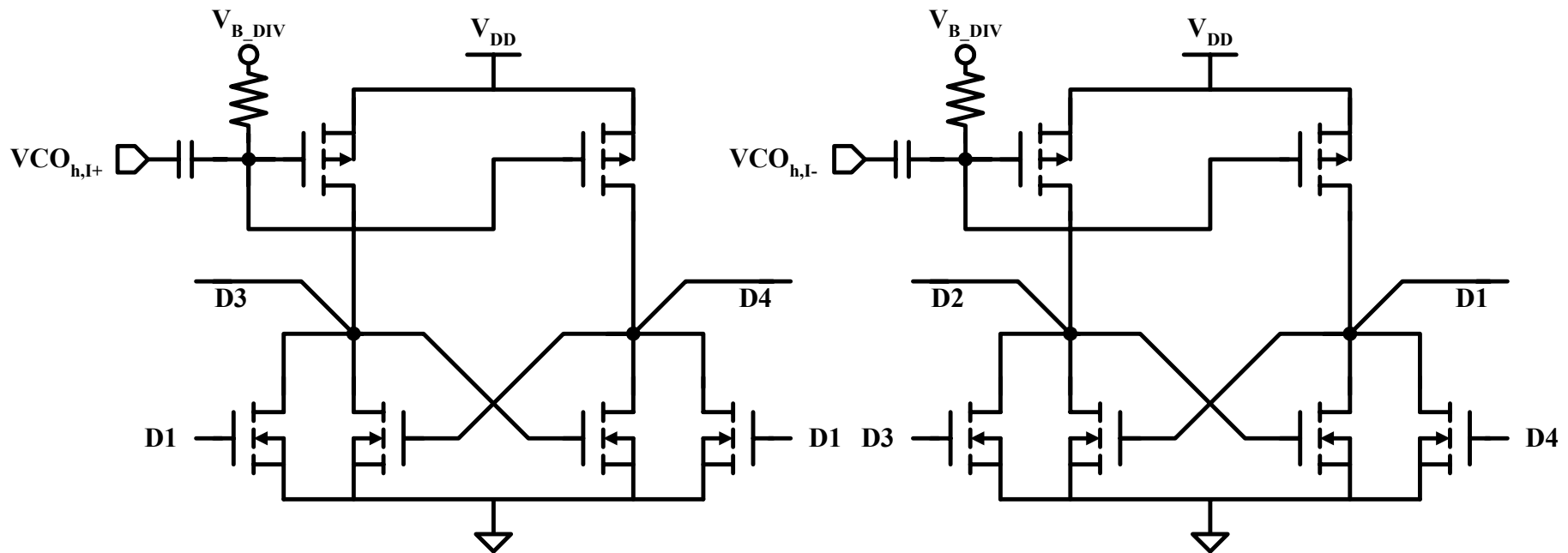
- Through a divided-by-2 circuit, the 3 GHz to 5 GHz can be designed
- The frequency gap from 5 GHz to 6 GHz are going to be reduced.



- Hence, oscillator operates from 3 GHz to 10 GHz can be realized.

Case II : Wide Tuning Range VCO for UWB

■ Simulation results: VCO tuning curve

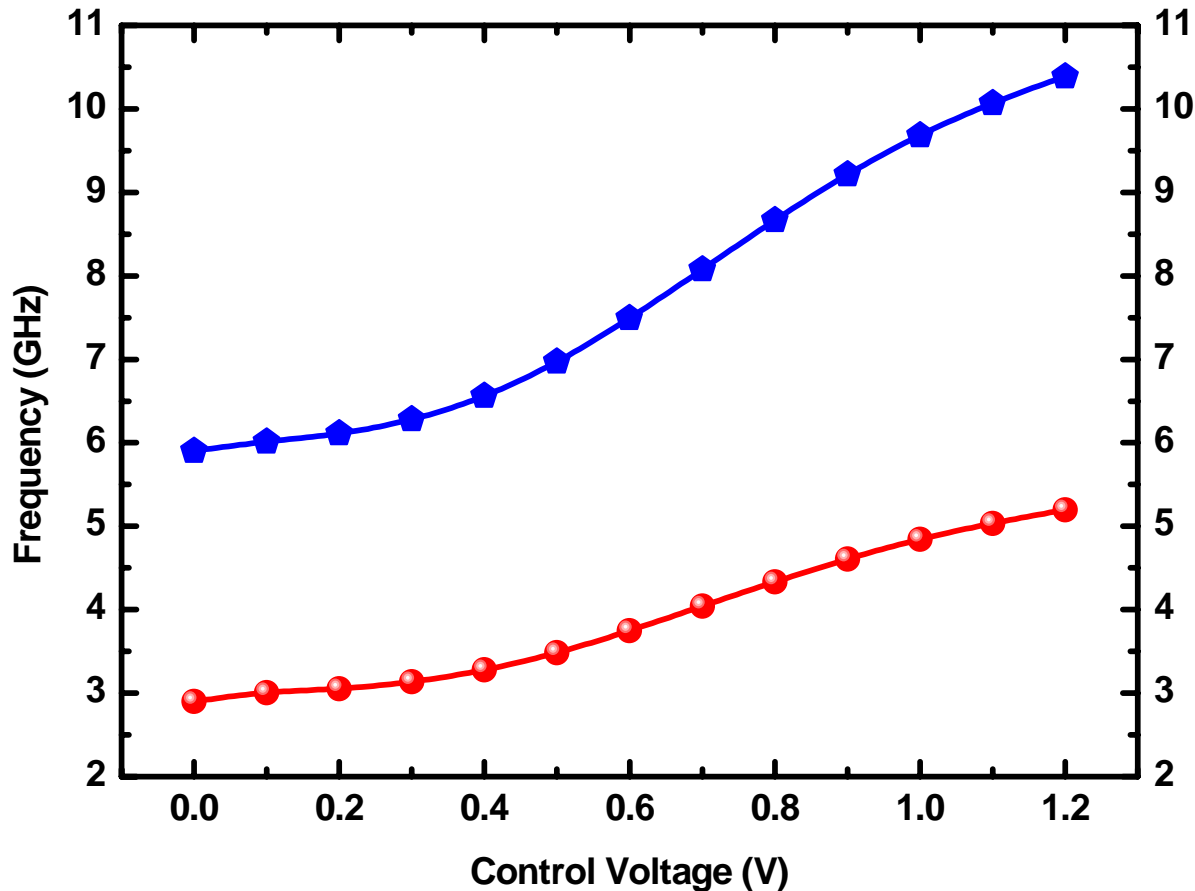

Conclusions

- **Ansoft HFSS helps extract parasitic and consider inter-connection in detail.**
- **Ansoft Designer/Nexxim has much higher simulation speed and higher capacity to handle larger circuits including N-port S-parameters extracted from EM. More realistic design and faster design period can be achieved.**
- **Ansoft Designer/Nexxim + HFSS is promising for the CMOS RFIC design flow.**